

N9/24f
2022EE91192

INDIAN INSTITUTE OF TECHNOLOGY ROPAR
GE108: Basic Electronics
Mid-Semester Examination

Max. Marks: 50

Duration: 2 Hours

Question I: Consider the circuit shown in Fig.1 with one practical diode, one capacitor and one 5 V DC supply. Assume that conducting diode exhibits a constant voltage drop of 0.7 V. Sketch and label output voltage for input shown. Please present necessary calculation and simplify circuits to justify output voltage levels. [6 pts]

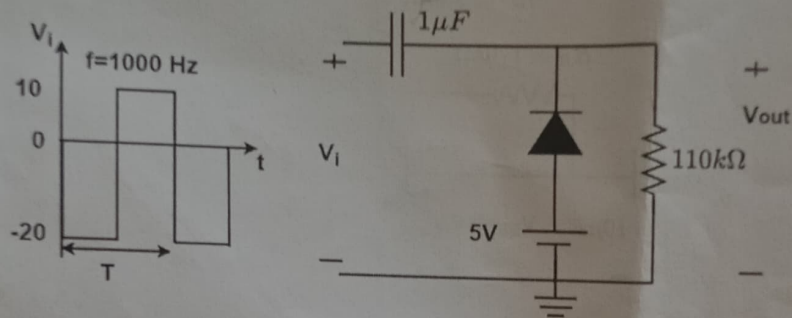


Fig.1: Diode circuit for Q-I

Question II: Consider the circuit shown in Fig.2 with one practical diode, two resistors and one 1V DC supply. Assume that conducting diode exhibits a constant voltage drop of 0.7 V. Sketch and label output voltage for input shown. [6 pts]

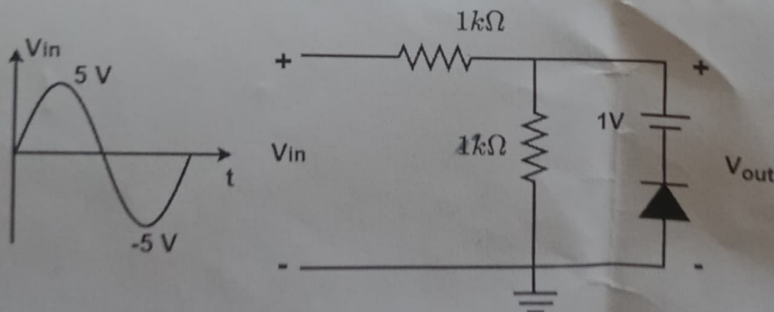


Fig.2: Diode circuit for Q-II

Question III: The BJT in the circuit of Fig. 3 has a β value of 200. Please answer the following questions:

- What is the name of the BJT configuration? [1 pt]
- What is the role of the R_B resistance in this circuit? [2 pts]
- Calculate the values of V_{CE} and I_C . What is the operating region of the BJT? [2 pts]
- Plot the quiescent (Q) point position on the load line for the above circuit. [2 pts]

- (e) Calculate the quiescent point when β becomes 50% greater than the given value above and comment on the sensitivity of the circuit to the change in β . [2 pts]
- (f) Find the voltage gain, input resistance, and output resistance values at the Q-point in question 3(d). [8 pts]
- (g) Why is it necessary to operate the BJT in the active region for amplifier circuits? [3 pts]

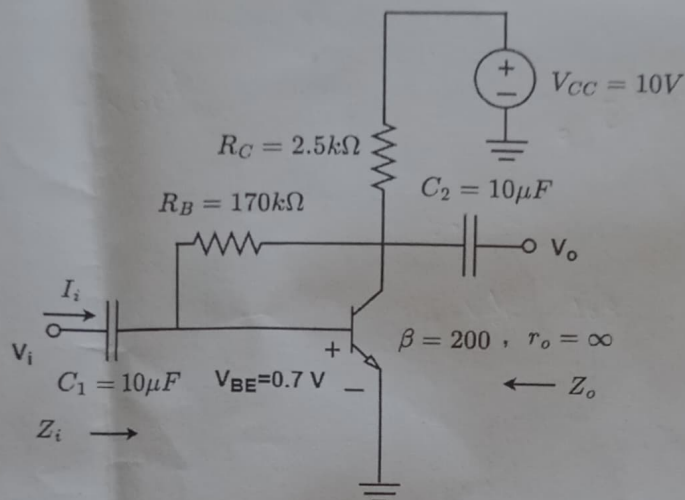


Fig. 3: Capacitively Coupled BJT Circuit for Q-II

Question IV: For the three circuits shown in Fig. 4, find the label node voltages and the operating region of BJTs. Assume that $V_{BE} = 0.7$ V. [6+6+6 Pts]

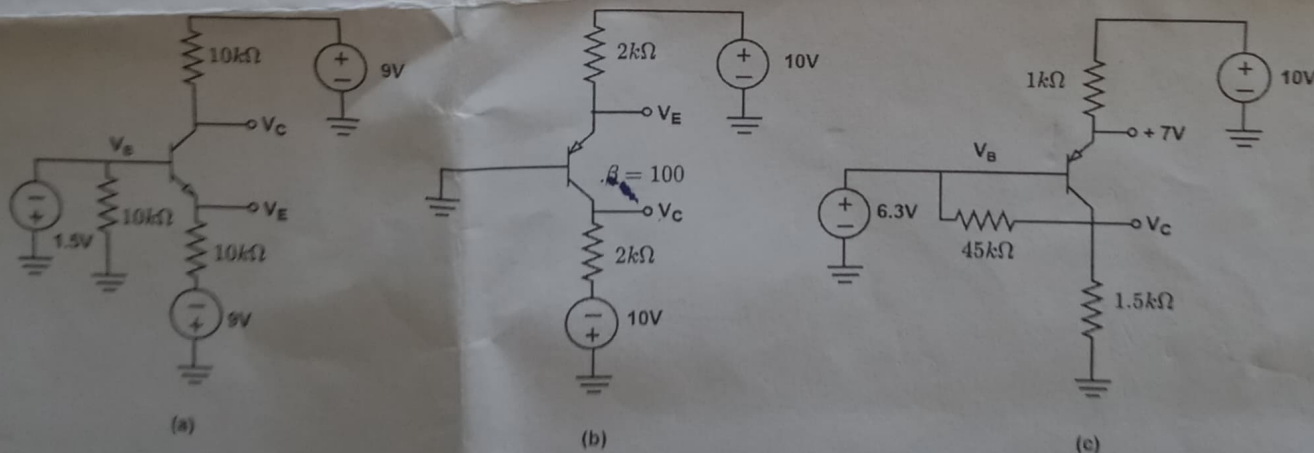


Fig. 4: DC-biased BJT Circuits for Q-IV

Na/cup
2022 EE 61192

INDIAN INSTITUTE OF TECHNOLOGY ROPAR
GE108: Basic Electronics
End-Semester Examination

Max. Marks: 65

Duration: 3 Hours

Question I: Consider the circuit shown in Fig. 1 with three ideal op-amps and resistors. Given that $V_1 = 5\text{ V}$, $V_2 = 4.75\text{ V}$, $R_1 = 1\text{ k}\Omega$, $R_2 = 49\text{ k}\Omega$, $R_3 = 10\text{ k}\Omega$ and $R_4 = 10\text{ k}\Omega$. Please find the output voltage (V_o) and justify the role of each op-amp configuration. [6+2 pts]

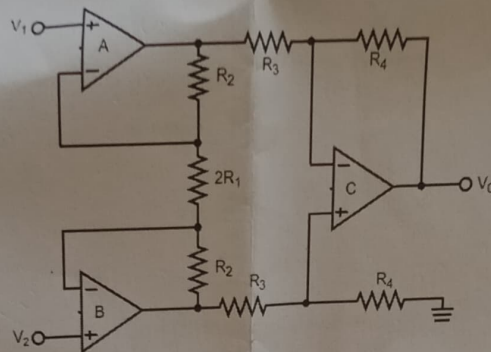


Fig.2: Circuit for Question-I

Question II: Consider the circuit shown below with three op-amps, two capacitors and six resistors. [8+2+2 pts]

- Calculate the overall transfer function (V_o/V_i).
- Explain the role of each op-amp configuration.
- Name the type of filter designed using the three-stage op-amp.

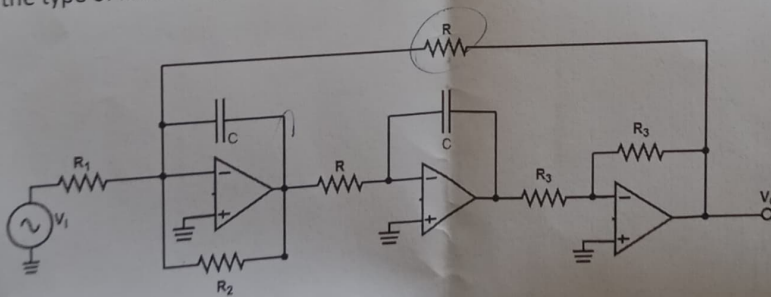


Fig.2: Circuit for Question-II

Question III: The MOSFET in the circuit of Fig. 3 has the following values: transconductance (g_m) = 0.5 mA/V , drain-to-source current (I_{DS}) = 0.5 mA , $\mu_n C_{ox}$ = $12.5\text{ }\mu\text{A/V}^2$, threshold voltage (V_{TH}) = 1.5 V , and surface mobility of electrons (μ_n) = $450\text{ cm}^2/\text{V-s}$. [2+3+4+4+4+3+3+4 pts]

- What is the name of the amplifier configuration?
- Find out V_D , V_S , and V_{GS} for below circuit?

- (c) Plot the quiescent (Q) point position on the load line for the above circuit. Determine the maximum range of allowed input small signal voltage (V_{sig}) for this amplifier.

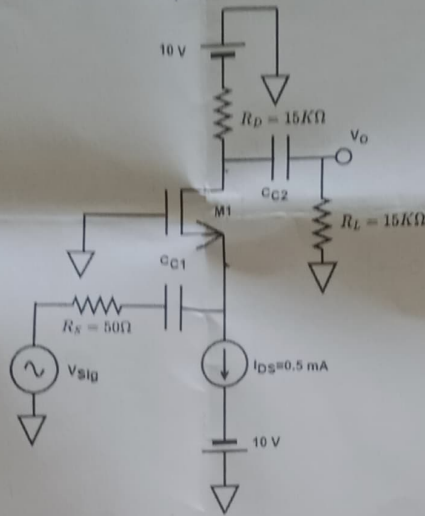


Fig. 3: Capacitively Couple MOSFET Circuit

- (d) Find the input and output resistance in the circuit.
 (e) Calculate the value of open-circuit voltage gain and overall voltage gain.
 (f) Describe a practical use for this circuit and explain its suitability for that application.
 (g) What is the role of I_{DS} current source in this circuit?
 (h) What is the difference between the saturation regions in MOSFET and BJT?

Question IV: For the three circuits shown in Fig. 4, find the label node voltages, label current values, and the operating region of MOSFETs. The transistors are characterized by $\mu_n C_{ox} = 2.5 \mu A/V^2$, $\mu_p C_{ox} = 20 \mu A/V^2$, $V_{TH,n} = 1 V$, $V_{TH,p} = -1 V$, $(W/L)_n = (W/L)_p = 3$, and $\lambda_n = \lambda_p = 0$, where n and p indicate n-type and p-type MOSFETs. [6+6+6 pts]

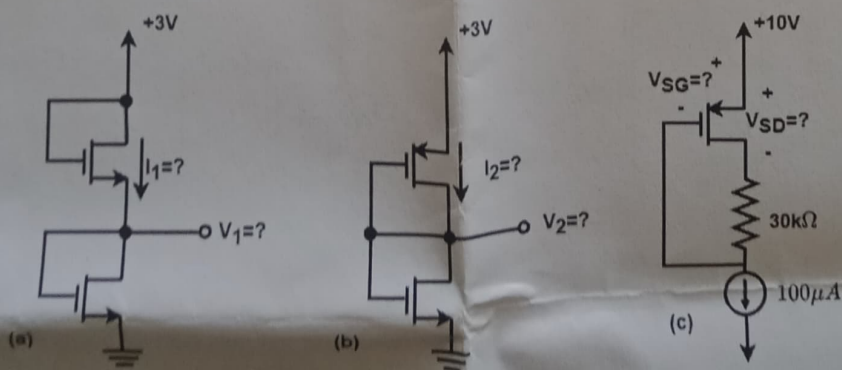


Fig. 4: DC-biased MOSFET Circuits