

metal oxide semiconductor field effect transistor

↑
construction

↑
working → electric field

we know

$$V = - \int \vec{E} \cdot d\vec{l}$$

due to electric field → width of channel
(Path of I)

$$R_{ch} = \frac{l}{\sigma A}, \quad A \uparrow, R_{ch} \downarrow, I \uparrow$$

I is controlled by E-field or voltage.

- it is also known as voltage controlled current source.

MOSFET have 4 terminals

- Source
- Drain
- gate → control terminal → It generate E-field to control I flow b/w source & drain
oxide (SiO_2)
 $V_g = 0$

metal oxide semiconductor field effect transistor

↑ construction, ↑ working → electric field

we know

$$V = - \int \vec{E} \cdot d\vec{l}$$

due to electric field → width of channel
(path of I)

$$R_{ch} = \frac{l}{\sigma A}, \quad A \uparrow, R_{ch} \downarrow, I \uparrow$$

I is controlled by E-field or voltage.


- it is also known as voltage controlled current source.

MOSFET have 4 terminals

- Source
- Drain
- gate → control terminal → Pt generate E-field to control I flow b/w source & drain
oxide (SiO_2)
 $V_g = 0$

- Input impedance of MOSFET is around $10^9 \Omega$
- it is smaller in size than BJT
- But $A_v(\text{Mos}) < A_v(\text{BJT})$ $A_v = \text{voltage gain.}$

MOSFET type

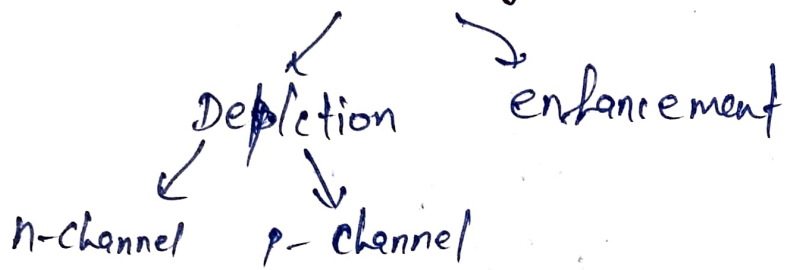

a) Depletion type


• n-channel

- $W_{\text{oxide}} \approx 1000 \sim 2000 \text{ \AA}$
- it is symmetrical device
Drain & Source can be interchanged.

• $Z_{in} = \text{high}$

- b/w gate & body it act as capacitor
- MOSFET is unipolar device

• Gen. we use Common Source

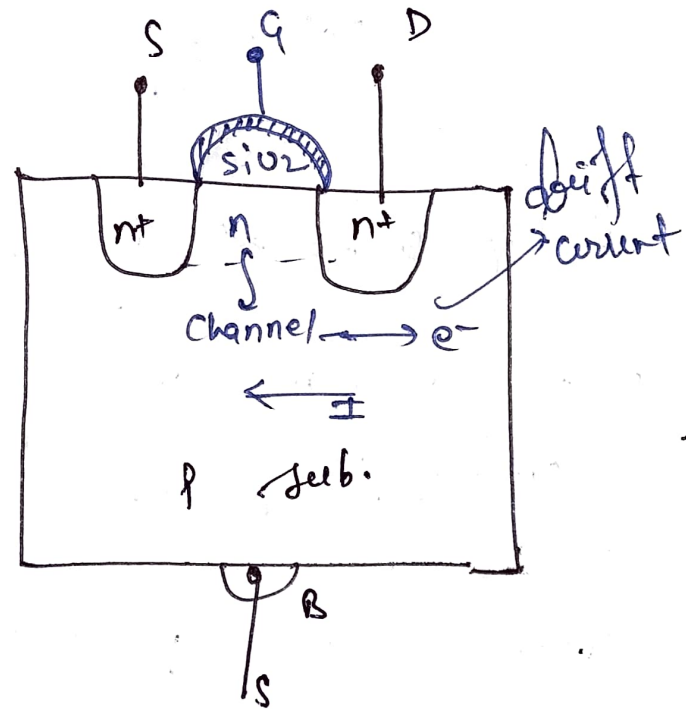

Case I :-

(3)

$$V_{GS} = 0, V_{DS} = 0$$

$$I_{DS} = 0, I_D = 0$$

drain to source current

Case II :-

$$V_{GS} = 0, V_{DS} > 0$$

$$I_{DS} > 0 \quad (\text{Drain to Source})$$

if

$$V_{DS} < 0$$

then current flow source to drain.

- MOSFET is bidirectional device.


Case III :-

$$V_{GS} < 0, V_{DS} > 0$$


As drain voltage is higher than source so channel vanish first from drain side.

when there is no channel

at this condⁿ is known as pinch off.

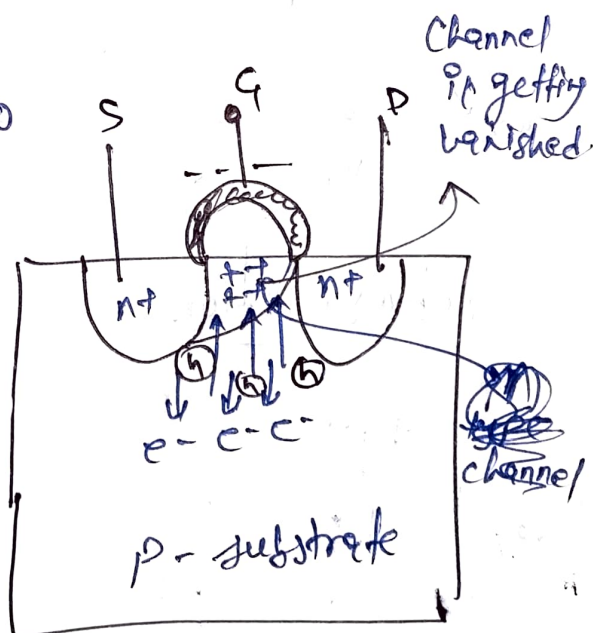

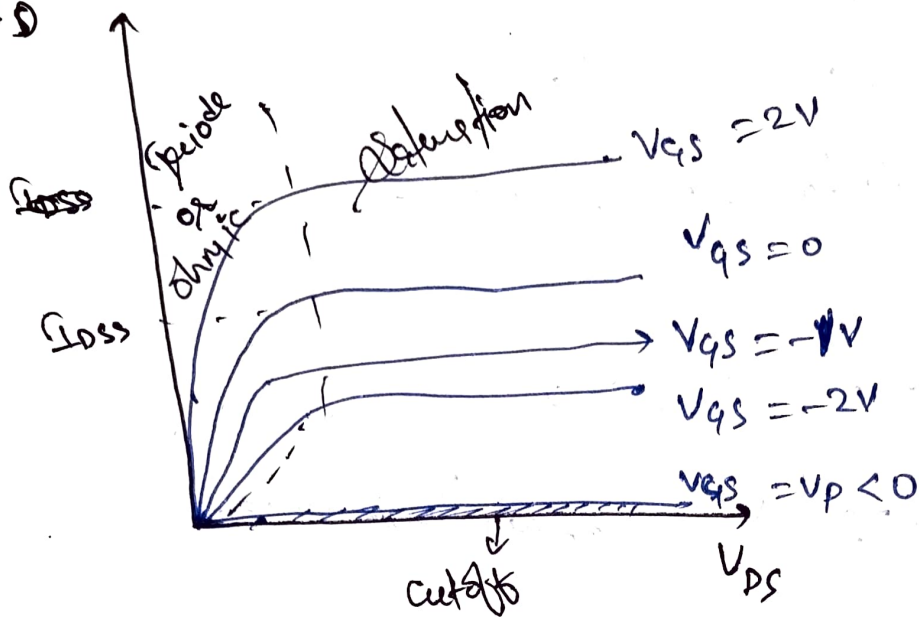
① output characteristics (characteristics)



if $V_{GS} < 0$
channel width reduces



$$R_{ch} = \rho \frac{L}{A} \uparrow$$

$I_D \downarrow$

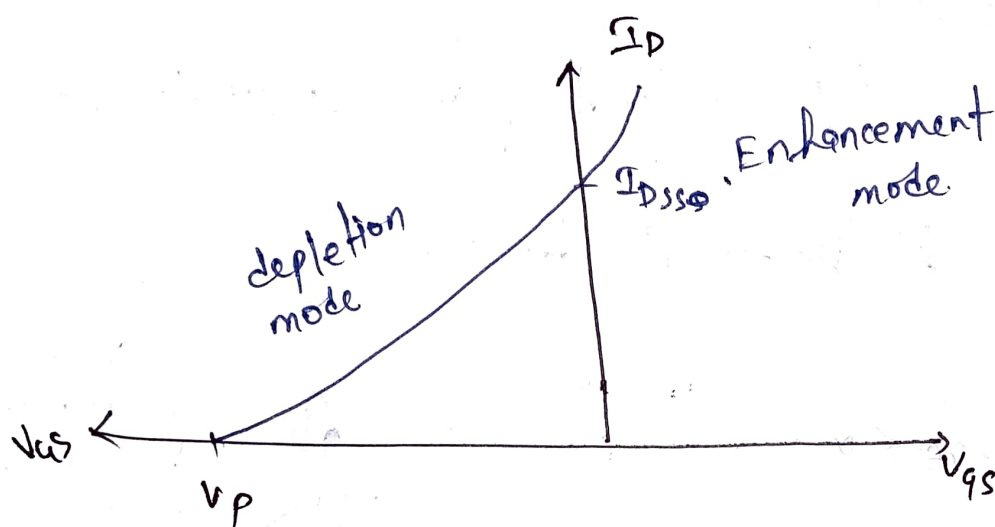

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

Representation

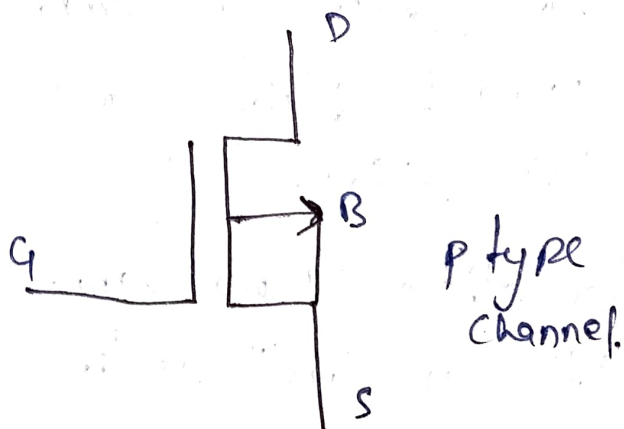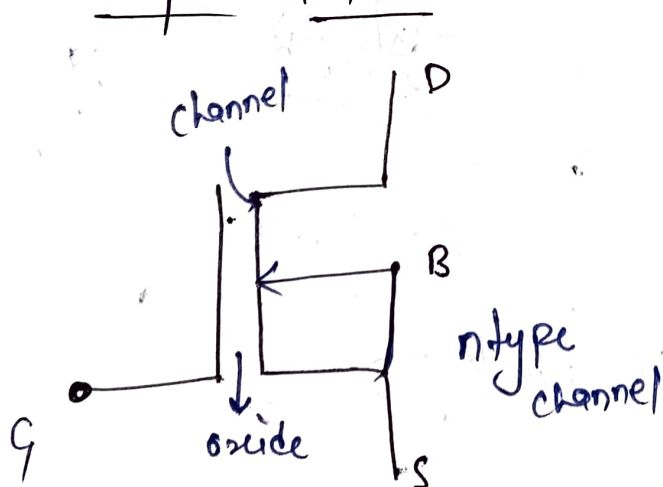

if body is shorted to source
then it act as 2 terminal voltage

← Region of operation: →

5

Pinch off voltage: $\Rightarrow$ Gate Source voltage at which no channel exist ($I_D = 0$)
threshold voltage:

• cut off region:

$$V_{GS} < V_T, I_D = 0$$

• Triode or ohmic region:

$$V_{GS} > V_T, V_{DS} \leq V_{GS} + |V_T|$$

$$I_D = \frac{1}{2} K \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$K_a = K_n \left(\frac{W}{2L} \right)$$

$$K_n = \mu_n C_{ox}$$

$$K = \mu_n C_{ox} \frac{W}{2L}$$

μ_n = mobility of e^-

C_{ox} = oxide capacitance (f/cm²)

W = channel width

L = channel length

Saturation region: $\rightarrow$

$$V_{GS} \geq V_T, V_{DS} \geq V_{GS} + V_T$$

$$I_D = K (V_{GS} + |V_T|)^2$$

When $V_{GS} = 0$, $I_D = I_{DSS}$


$$I_{DSS} = |K| V_T^2$$

$$K = \frac{I_{DSS}}{V_T^2}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_T} \right)^2$$

← Enhancement type MOSFET → $t_{ox} \rightarrow$ oxide width

- channel is not formed by doping
- fabrication cost is reduced.

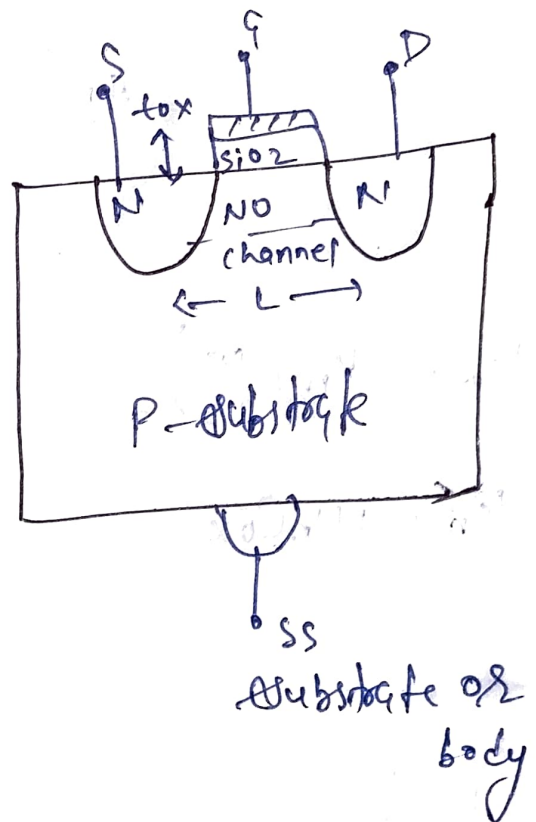

Case I

$$V_{GS} = 0, V_{DS} = 0$$

$$I_D = 0$$

Case II

$$V_{GS} = 0, V_{DS} > 0$$

no channel present hence

$$I_D = 0$$

Case 3:

when V_{GS} is varies

- Accumulation mode
- depletion mode
- Inversion mode.

Accumulation mode

when $V_{GS} < 0$

- P-type → majority: holes
- $F_n \rightarrow$ dirⁿ of E-field
- holes accumulate under gate
- no channel formation $I_D = 0$

depletion mode

when $V_{GS} > 0$

$0 < V_{GS} < V_T$
↓
depletion region

- hole is $\parallel$ to E-field
- hole move away from gate terminal.
- channel region is depleted of charge carriers.
- no channel formation, $I_D = 0$.

Inversion mode

$V_{GS} = \text{high} > 0$

~~$0 < V_{GS} < V_T$~~

- holes move away from channel
- minority carriers electrons moves toward gate terminal.
- An channel region when $\boxed{n > p} \rightarrow$ n-type material/
channel is formed.

threshold voltage: min. value of V_{GS} at which inversion take place.

$\frac{W}{L}$ = aspect ratio of Mosfet

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \text{ f/cm}^2 \text{ (Cap. per unit area).}$$

Region of operations: -

1) $V_{GS} < V_T$

• no channel is formed

$$I_D = 0$$

$$V_T > 0 \quad (\text{n-channel MOS})$$

I_D does not depend on V_{DS}

2) Linear or Triode region: -

$$V_{GS} > V_T$$

• channel is formed

then

$$V_{GS} < V_{GS} - V_T$$

$$I_D = \alpha K \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

saturation region:-

$$V_{GS} > V_T$$

$$V_{DS} > (V_{GS} - V_T)$$

Channel starts to vanish near drain

$$I_D = K [(V_{GS} - V_T)]^2$$

$$K = \mu_n C_{ox} \frac{W}{L} \left(\frac{A}{V^2} \right)_{\text{unit}}$$

as $V_{DS} \uparrow$, $L \downarrow$, channel length modulation

ideal

$$I_D = K (V_{GS} - V_T)^2$$

Practically

due to channel length modulation



$$I_D = f(V_{DS})$$

$$I_D = K (V_{GS} - V_T)^2 [1 + \lambda V_{DS}]$$


λ = channel length modulation

characteristics of n-mos


o/p charac

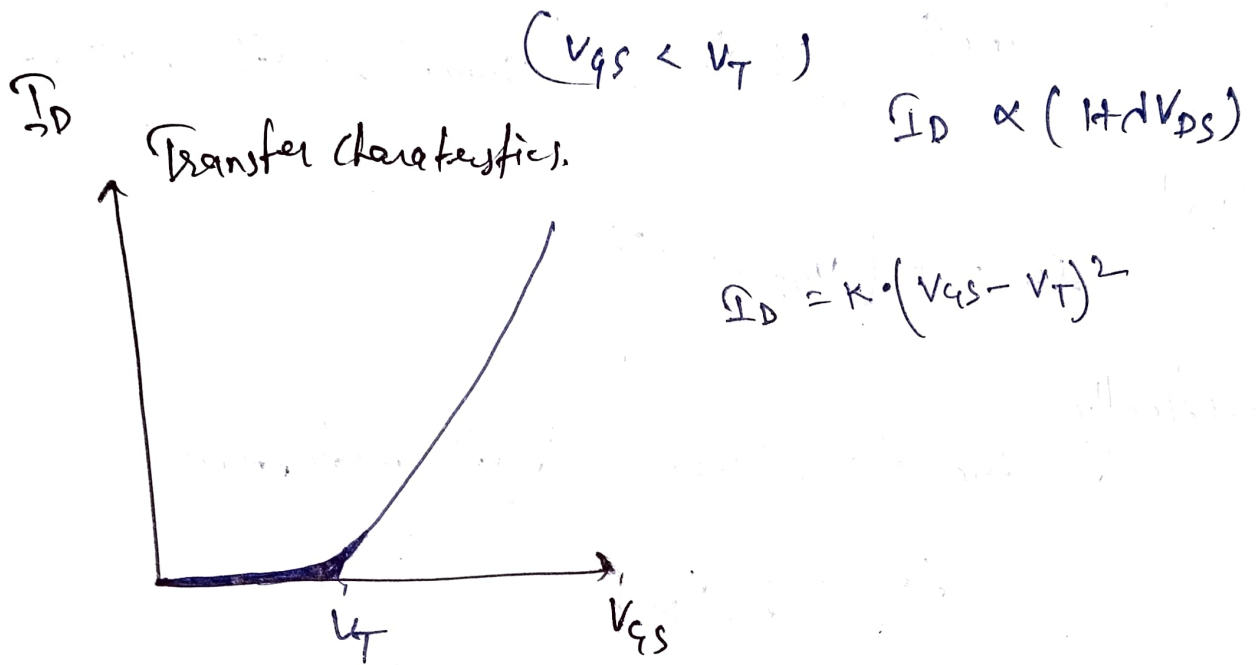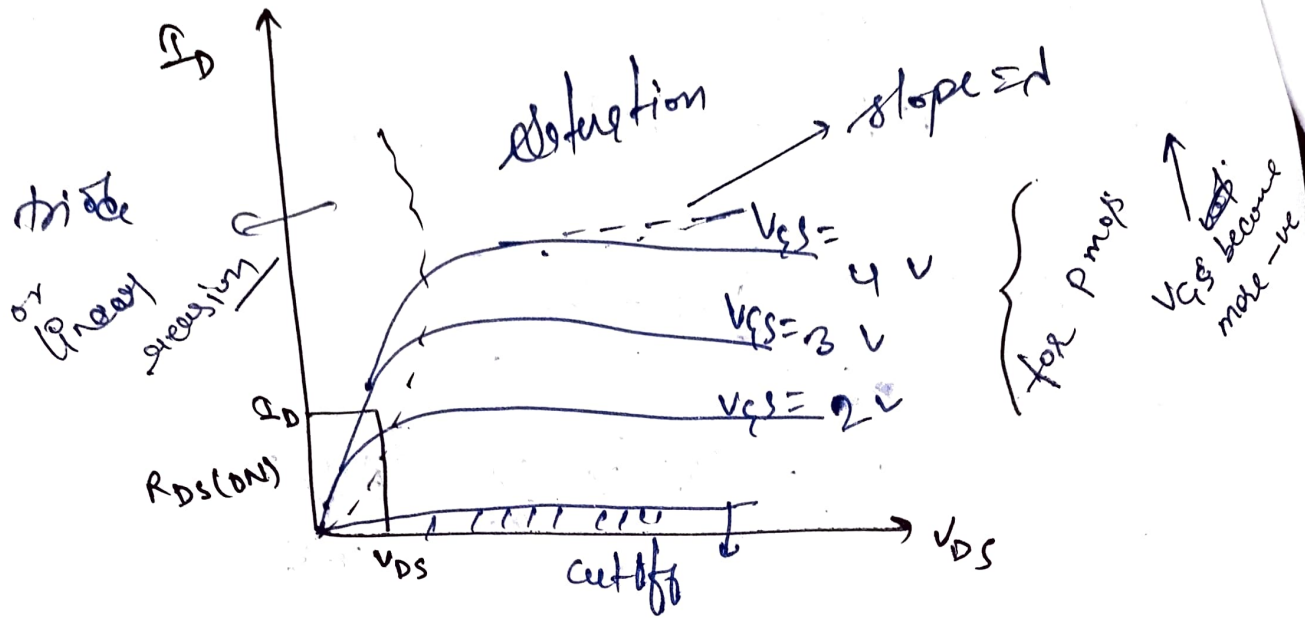


Enhancement type MOSFET symbol: —

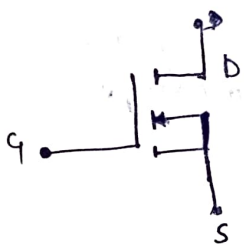

n-channel

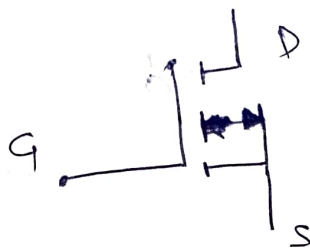

p-channel

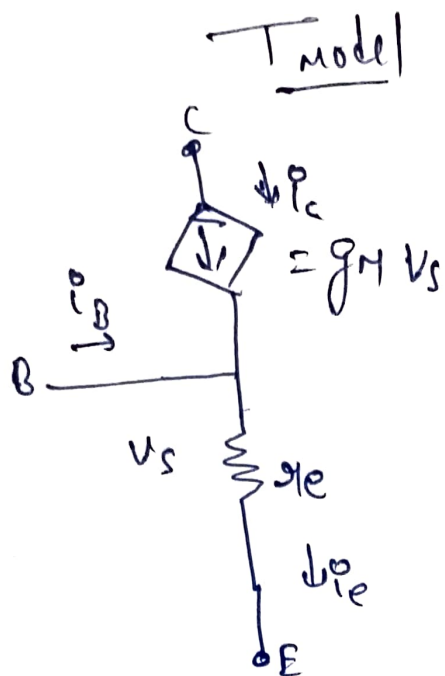

$$g_m = \frac{I_c}{V_T}$$

$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$

$$\alpha = g_m r_e$$

*

$$R_{in} = r_\pi$$

$$A_{v0} = -g_m R_c$$

$$R_o = R_c$$

$$A_v = \frac{A_{v0} R_L}{R_L + R_o} \quad \text{or} \quad -g_m (R_c \parallel R_L)$$

overall voltage gain

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_v$$

$$V_{sig} = \frac{R_{in}}{R_{in} + R_{sig}} \cdot V_\pi$$

$$V_o = G_v V_{sig}$$



$$V_{sig} = \frac{R_{in} + R_{sig}}{R_{in}} \cdot V_{\pi}$$

MOSFET AS SWITCH

MOSFET:- is a voltage control device, it can be used with microcontroller also.


More power efficient as compare to BJT

There are two type of losses when MOSFET OR BJT are used as switches:-


- conduction loss
- Switching loss
- MOSFET are more thermally stable as compare to BJT because MOSFET has +ve temp. Co-efficient

$$\text{As } T \uparrow \Rightarrow R_{DS(on)} \uparrow \Rightarrow I_D \downarrow$$

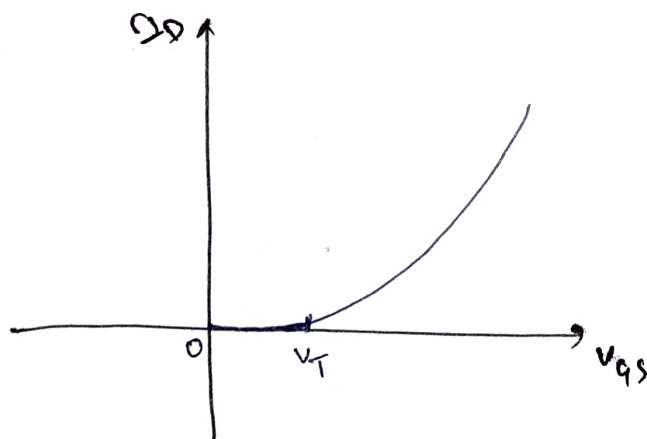- Enhancement type MOSFET are used for switches.




n type MOSFET

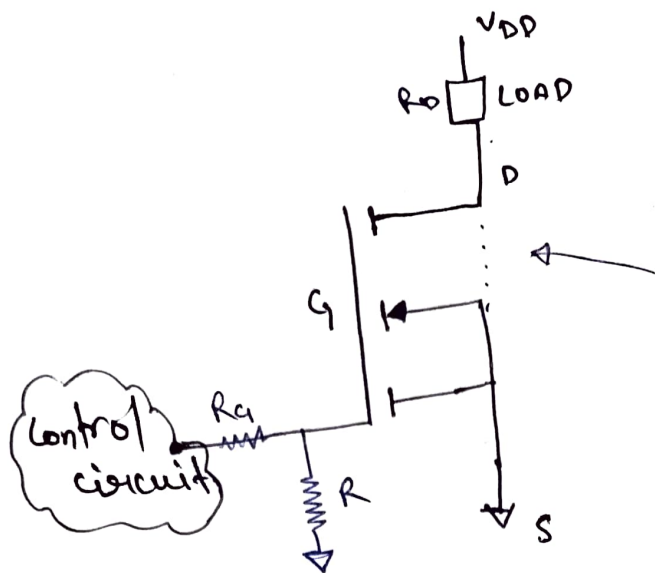

• when $V_{GS} < V_T$
no current flow (off)

• when $V_{GS} > V_T$
(closed ckt) (ON)

Gate to source ckt before R

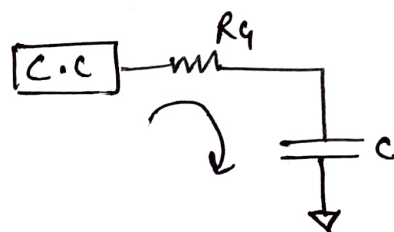




let load R_D , $V_{DS} = 0$

$$I_D = \frac{V_{DD}}{R_D}$$

if $I_D = 0$, $\Rightarrow V_{DS} = V_{DD}$

$\Rightarrow$ operating point


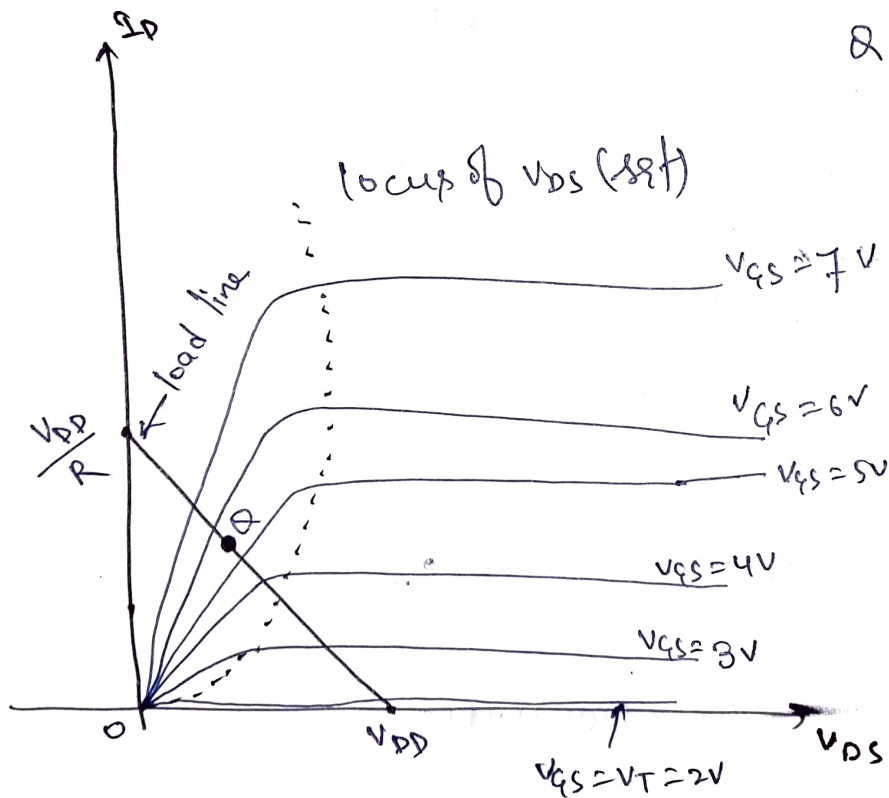


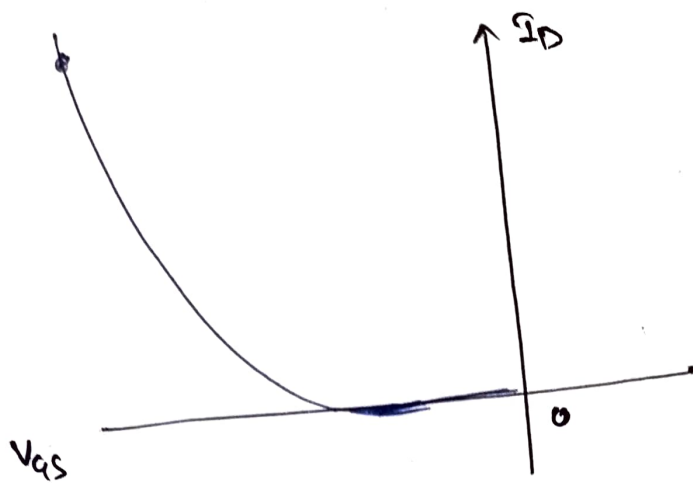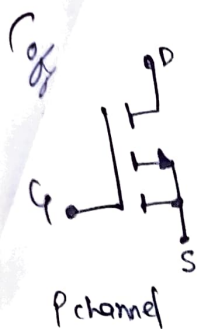

P-type MOSFET

As a switch.

$$V_{GS} = 0$$

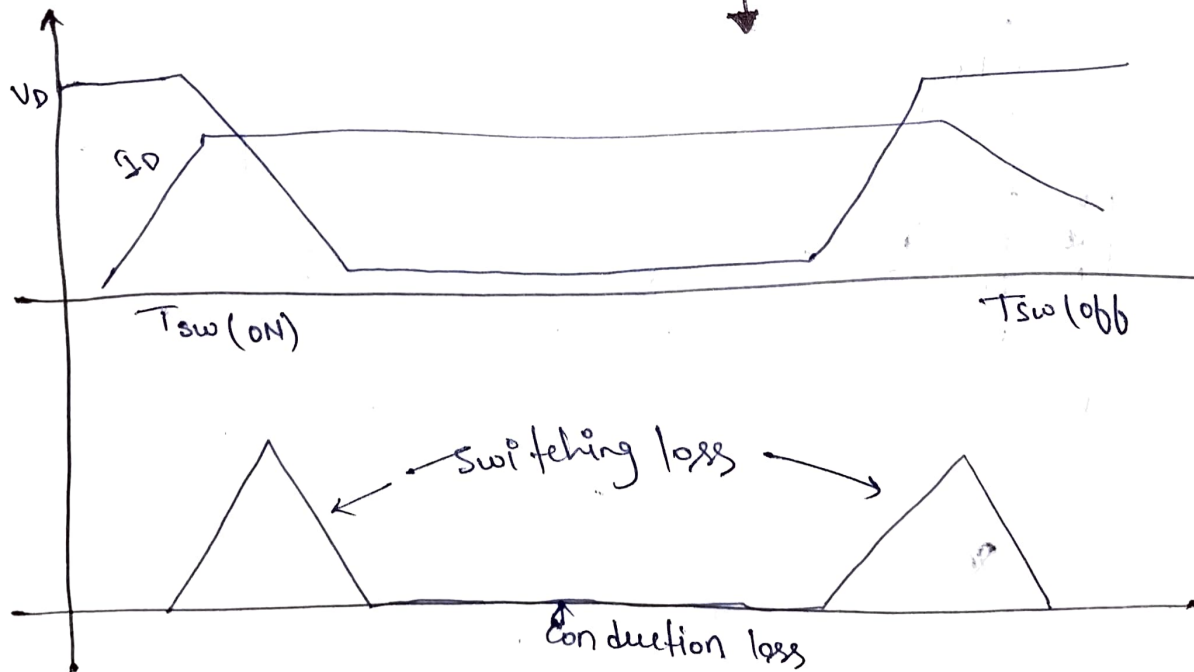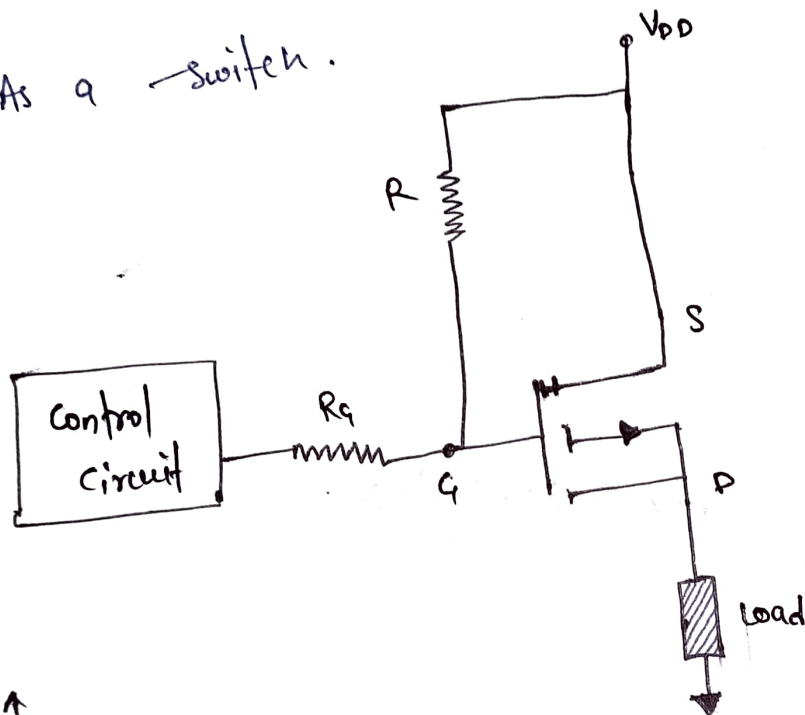

MOSFET Biasing Depletion Type MOSFET:

for n channel,

to be in saturation region (active mode)

$$V_{DS} \geq V_{GS} - V_p$$


$$|V_{GS}| < |V_p|$$

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2$$

there are three type of biasing can be done in MOSFET:-

- fixed biasing
- self biasing
- voltage divider biasing


Depletion type MOSFET (fixed biasing) :-

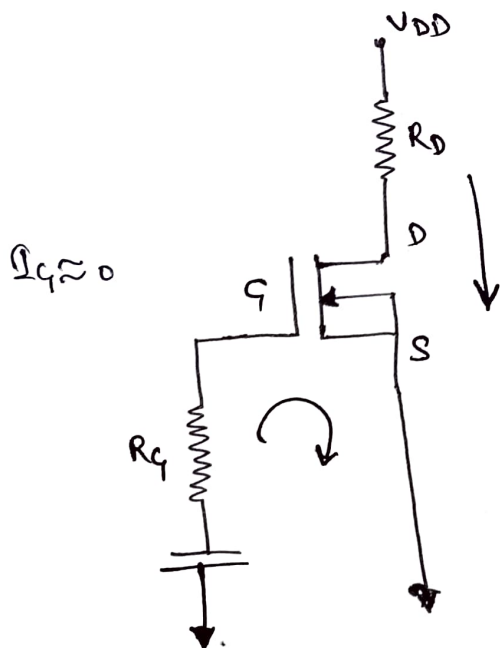


$$V_{GS} = -V_{GG}$$

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2 \quad (1)$$

$$V_{DS} = V_{DD} - I_D R_D \quad (2)$$

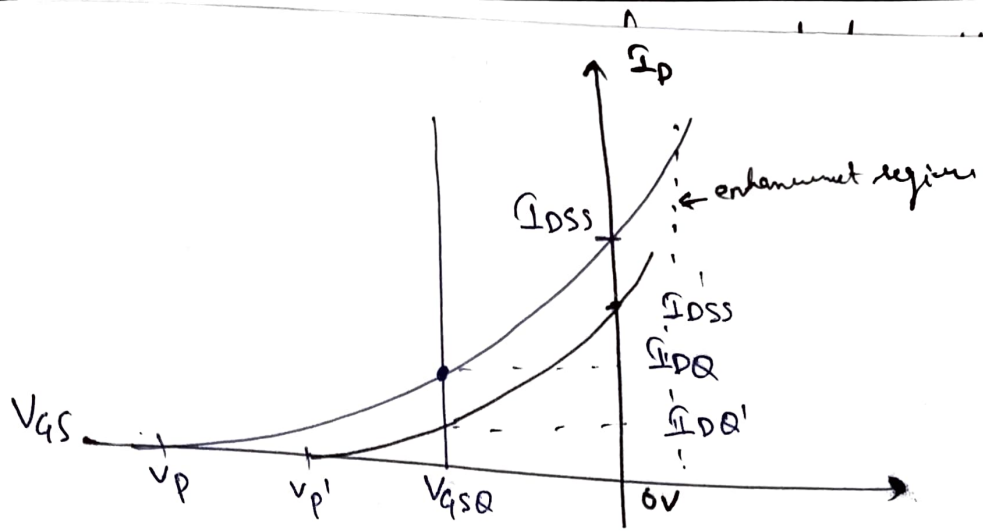


Depletion Type MOSFET (self Biasing):

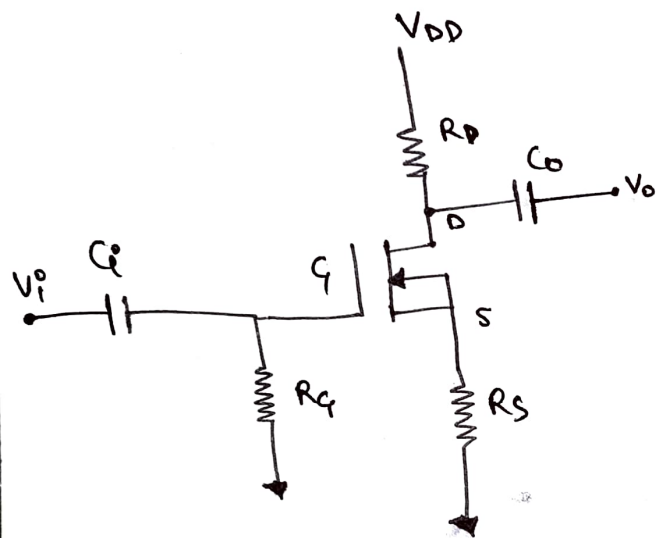

PS equⁿ


$\Rightarrow$

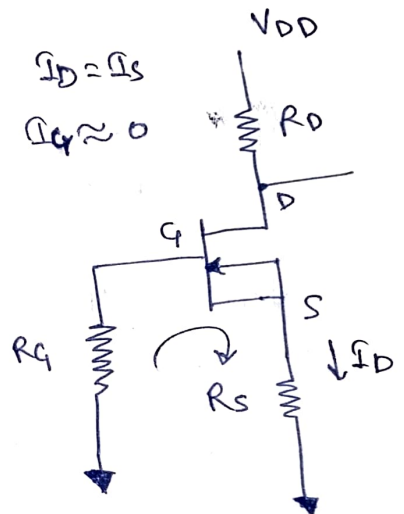


$$V_{GS} = -I_D R_S$$


$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

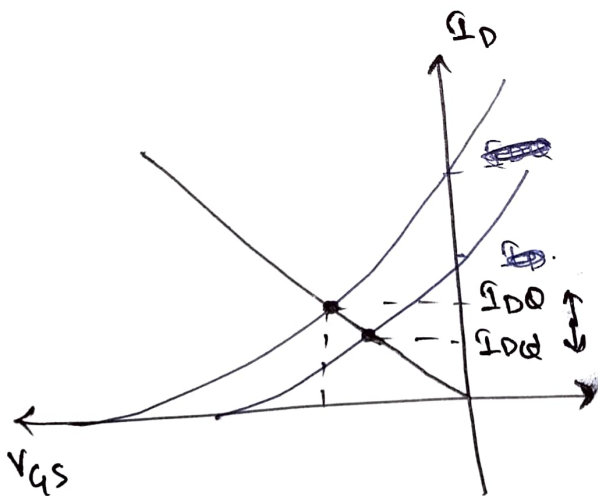

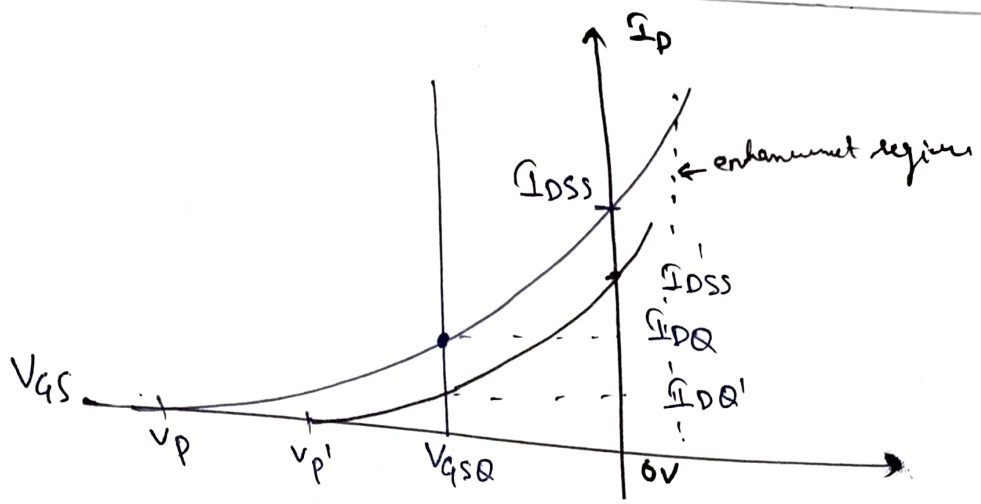


Depletion type MOSFET (self Biasing):

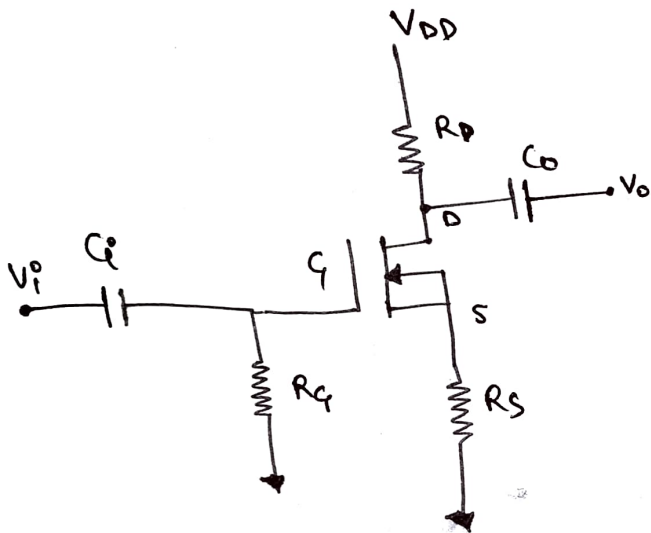



PS equⁿ

$\Rightarrow$

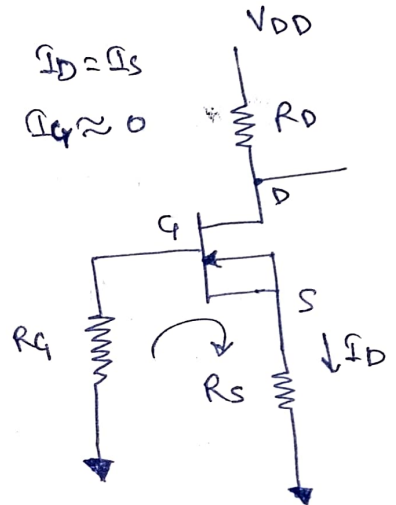


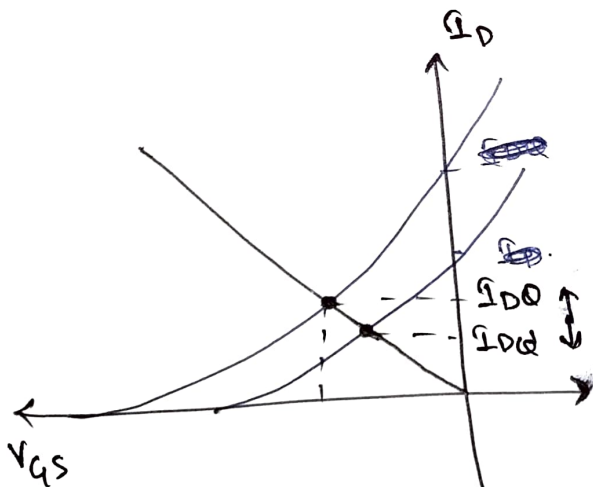- $V_{GS} = -I_D R_S$
- $I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$
- $V_{DS} = V_{DD} - I_D (R_D + R_S)$




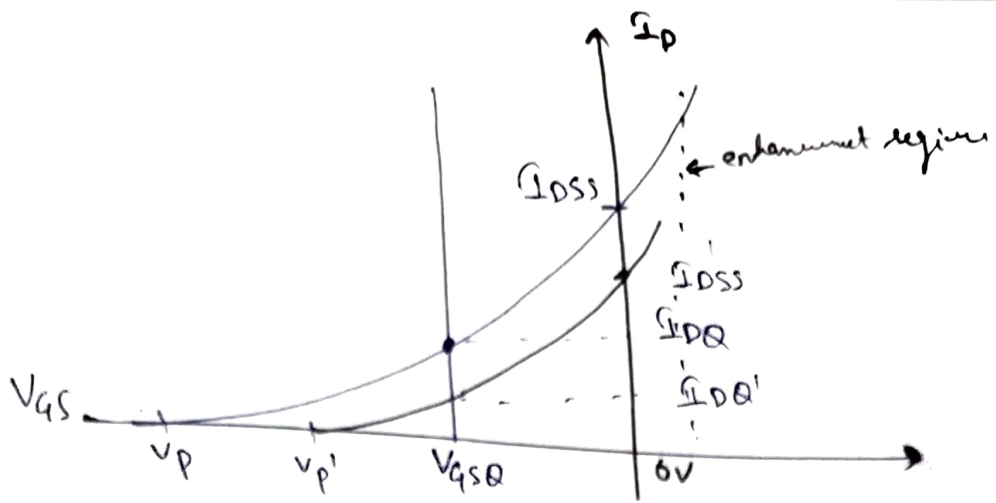


Depletion type MOSFET (self Biasing):

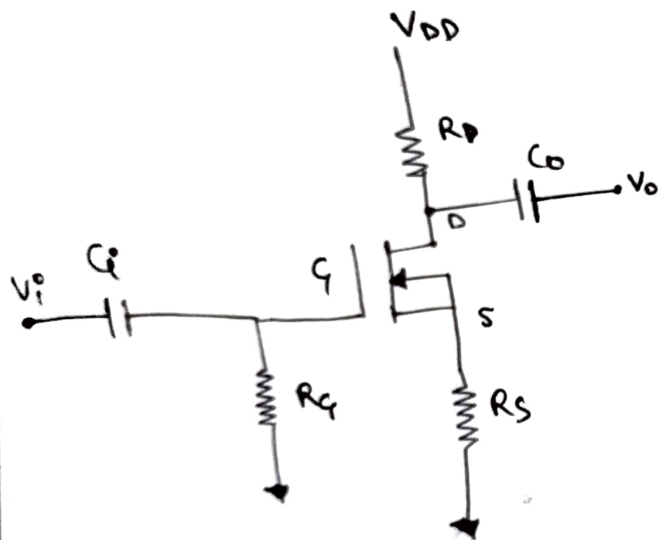


PS equⁿ
 $\Rightarrow$

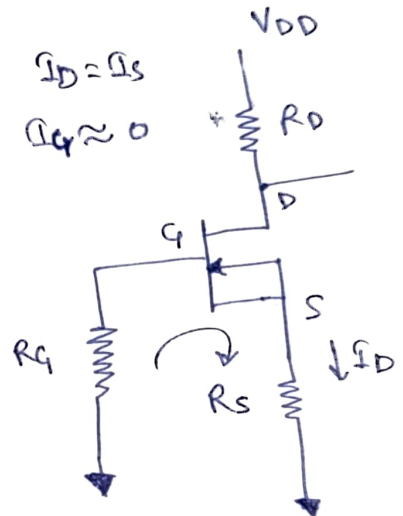

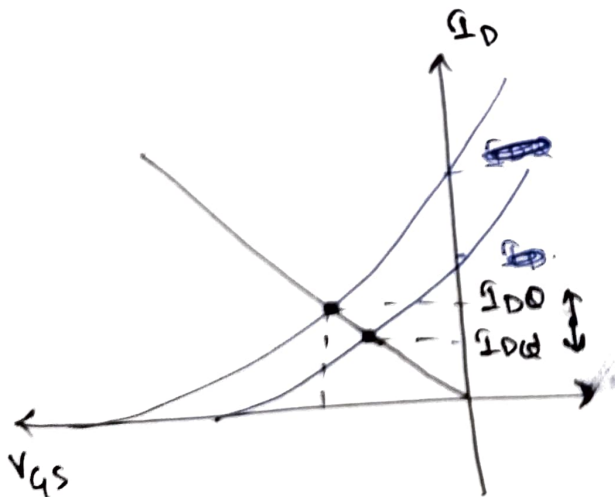
- $V_{GS} = -I_D R_S$
- $I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2$
- $V_{DS} = V_{DD} - I_D (R_D + R_S)$



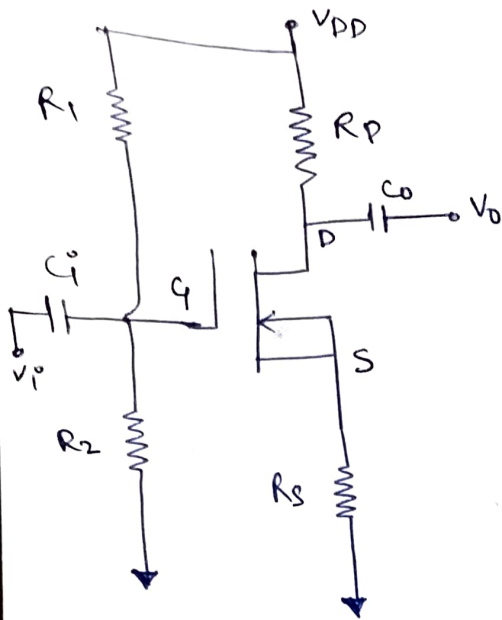Depletion type MOSFET (voltage divider Bias)



DC
⇒
eqn

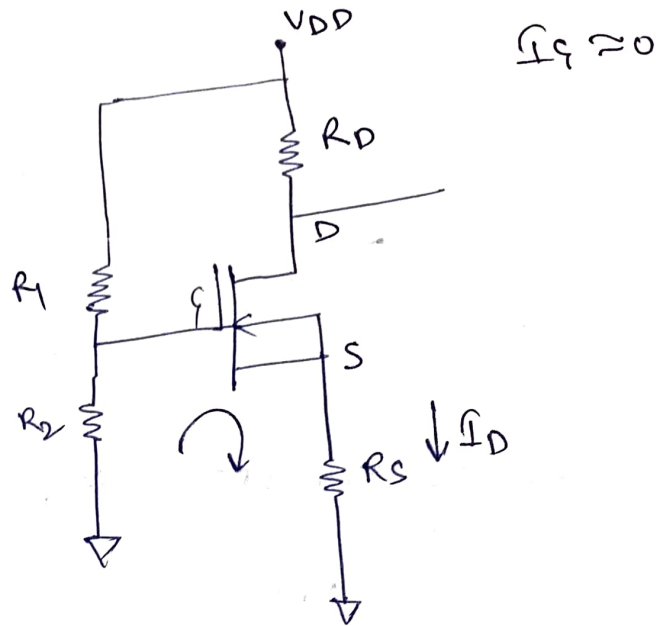


$$I_G \approx 0$$

$$V_G = \frac{R_2}{R_1 + R_2} \cdot V_{DD}$$

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

$$V_{GS} = V_G - I_D R_D$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

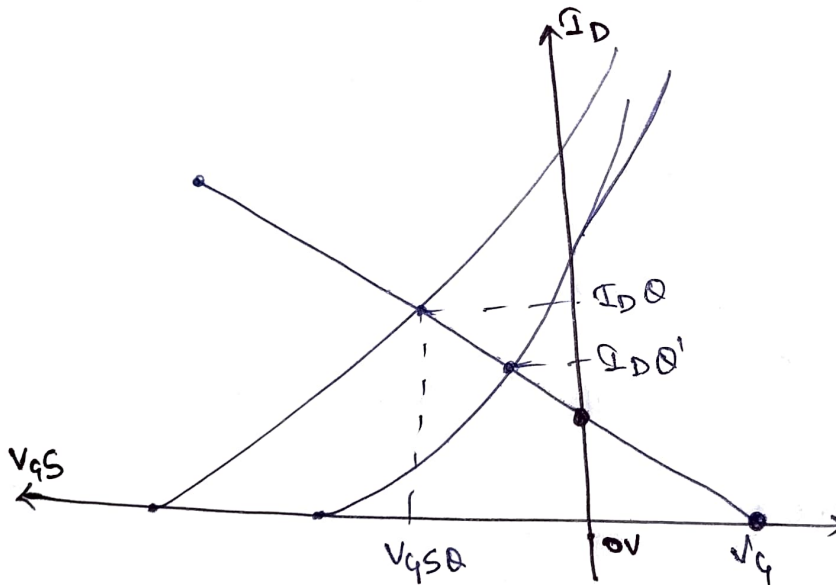


$$I_D = \frac{V_G}{R_S}$$


23

Enhancement type MOSFET


7.

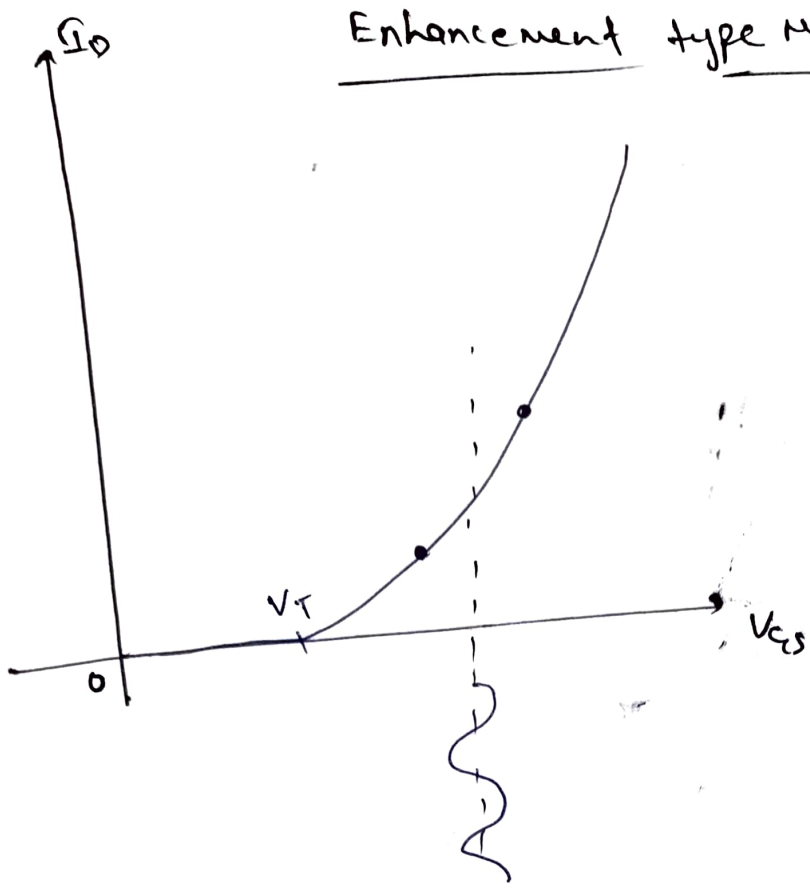

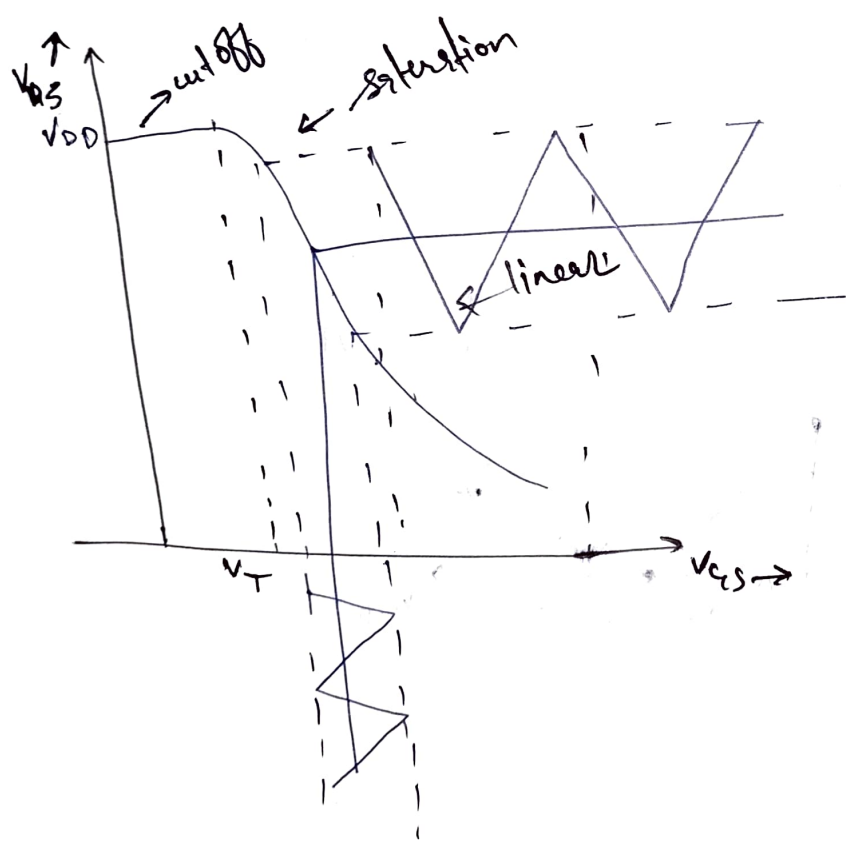voltage transfer characteristics of the MOSFET:-




MOSFET Biasing:-

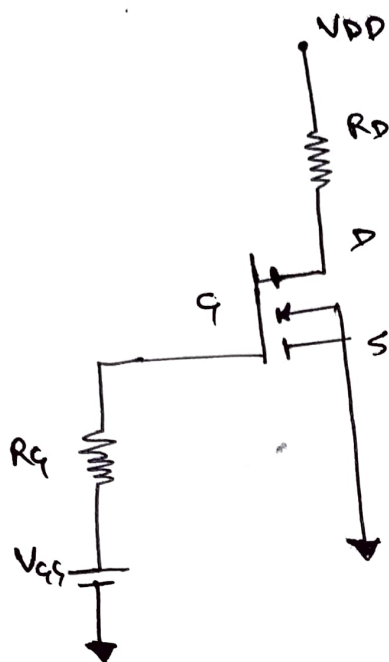


$$I_D = K(V_{GS} - V_T)^2$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2$$

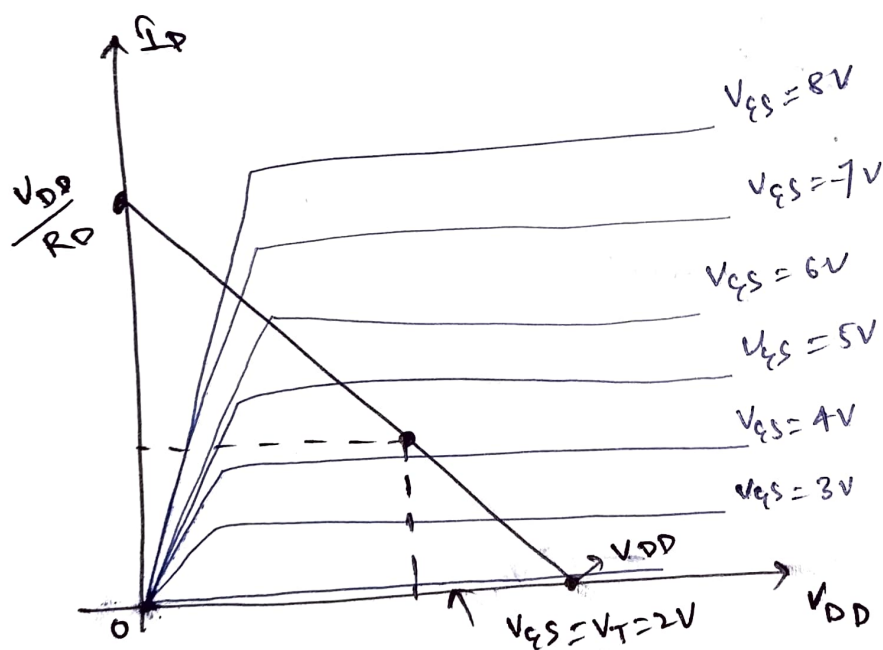
Enhancement type MOSFET (Drain characteristics):-



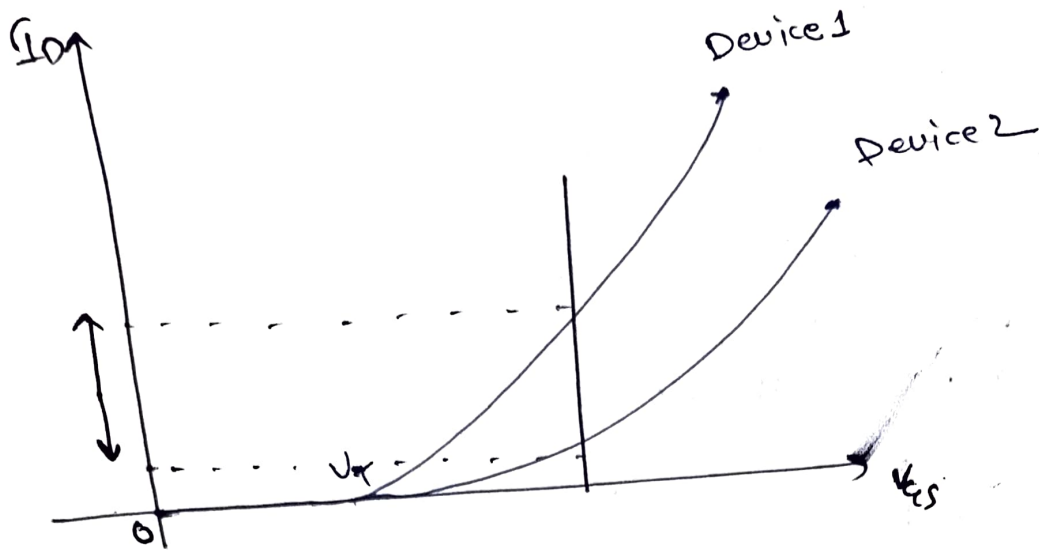Transfer characteristics of Enhancement type MOSFET 9.



Voltage Divider Biasing:-

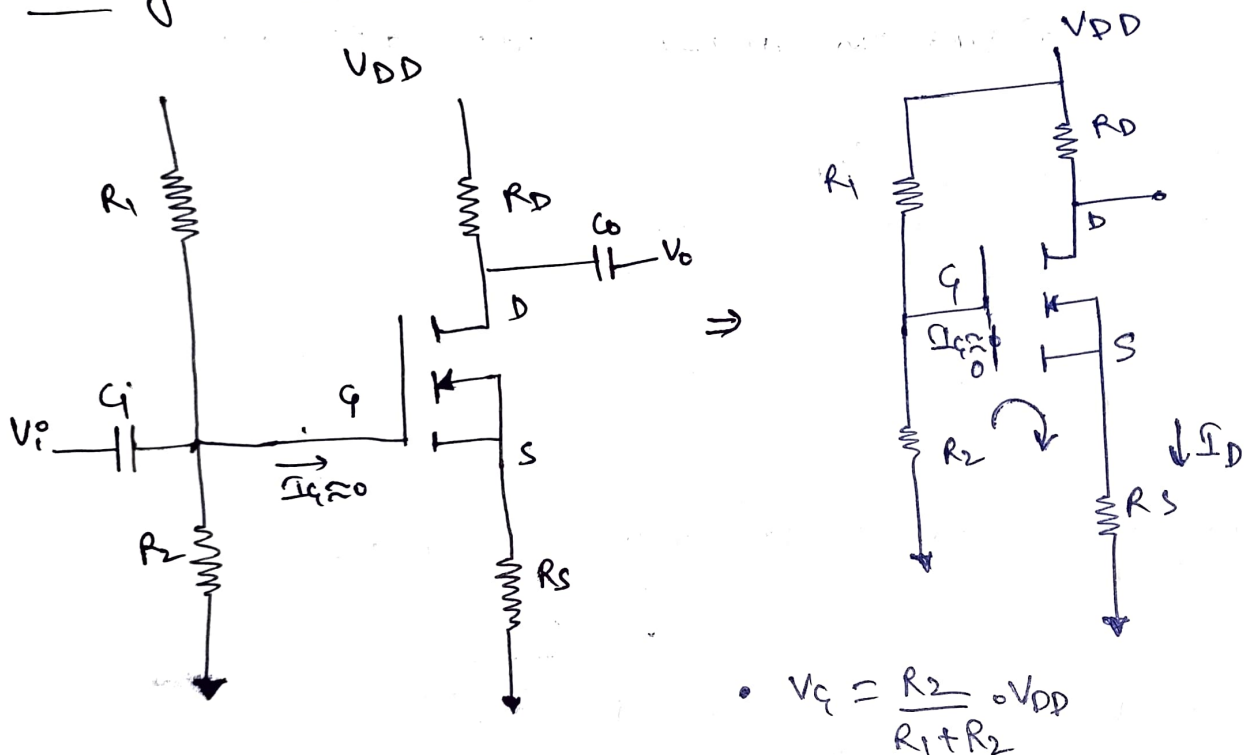


- $V_{GS} = V_G - I_D R_S$


- $I_D = K(V_{GS} - V_T)^2$

- $I_D = \frac{1}{2} \mu_n C_{ox} \left[\frac{W}{L} \right] (V_{GS} - V_T)^2$

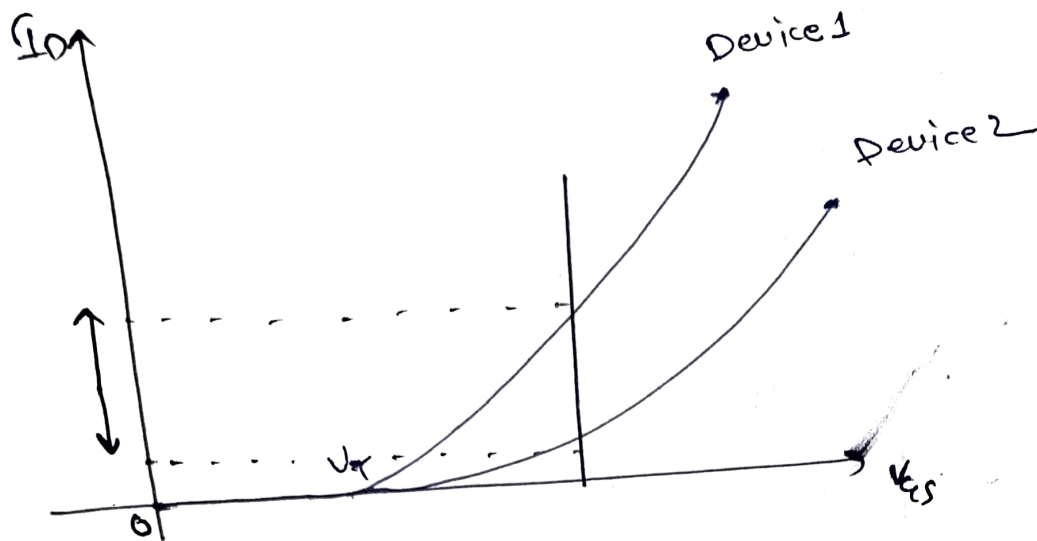Transfer characteristics of Enhancement type MOSFET 9.



Voltage Divider Biasing:-

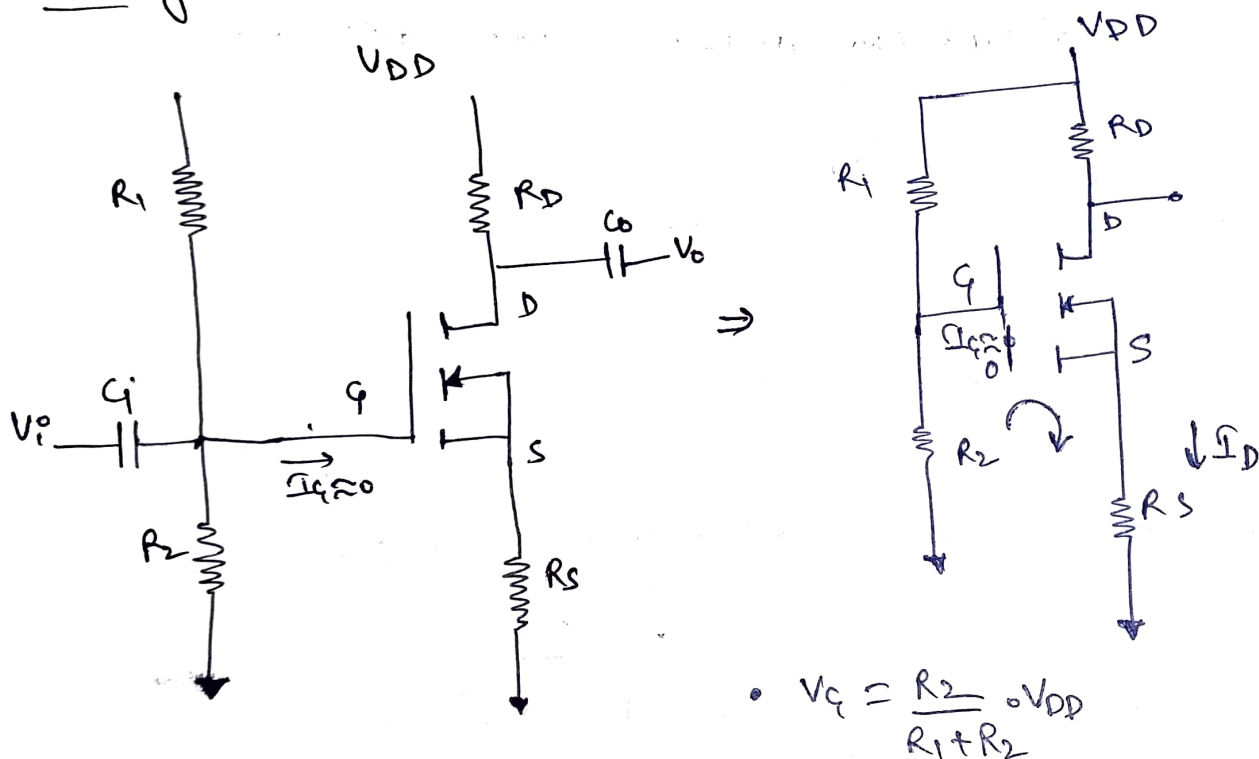


- $V_{GS} = V_G - I_D R_S$
- $I_D = K(V_{GS} - V_T)^2$

- $I_D = \frac{1}{2} \mu_n C_{ox} \left[\frac{W}{L} \right] (V_{GS} - V_T)^2$

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

Drain feedback biasing: —

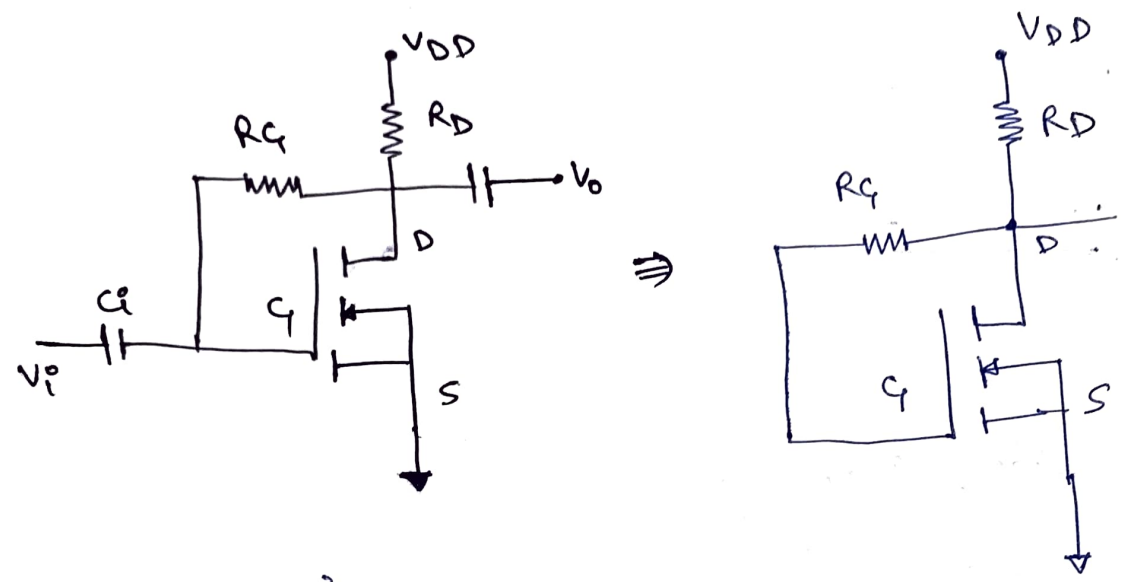

$$I_D = K(V_{GS} - V_T)^2$$


- $V_D = V_G$
- $V_{DS} = V_{GS} = V_{DD} - I_D R_D$

In ~~sat~~ mode.


$$I_D = \frac{1}{2} \mu_n C_{ox} \left[\frac{W}{L} \right] (V_{GS} - V_T)^2$$

$$V_{GS} = V_{DD} - I_D R_D$$

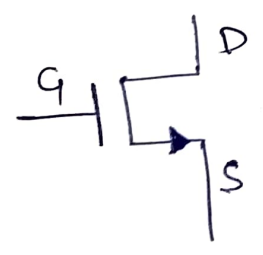Enhancement type MOSFET another symbol/p: —




N-channel MOSFET

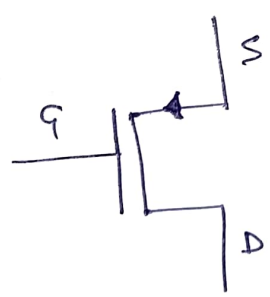


P-channel MOSFET

channel length modulation. :-

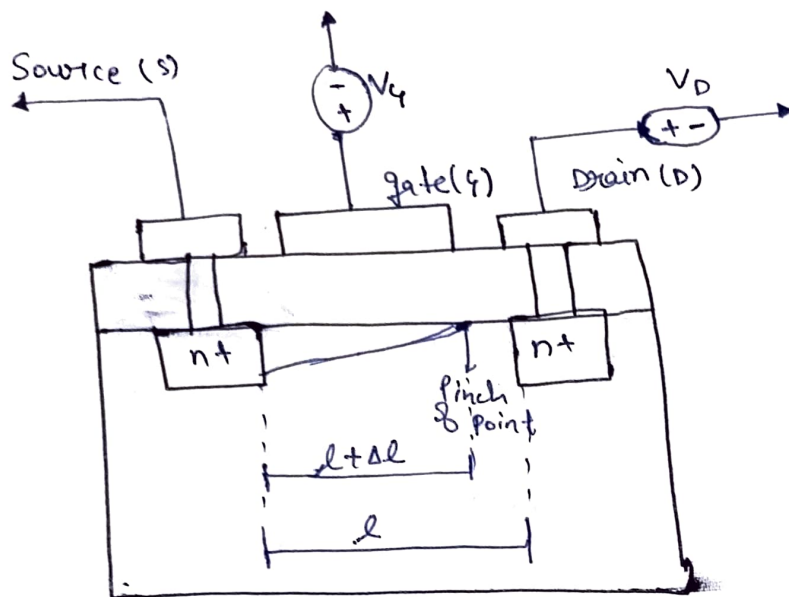

$$V_{DS} \geq V_{GS} - V_T$$
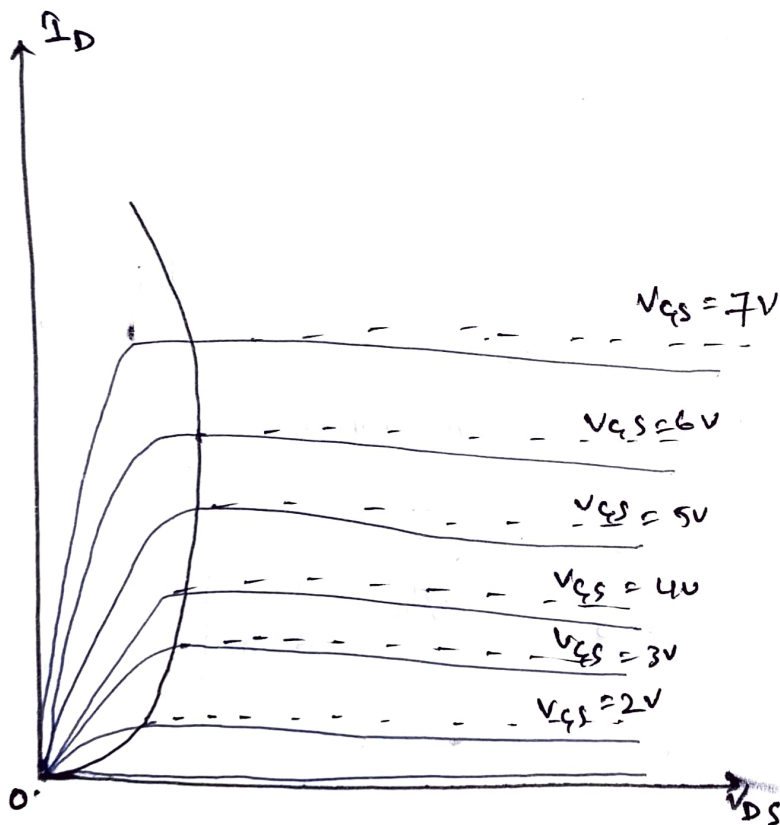
$$I_D = \frac{1}{2} \mu_n C_{ox} \left[\frac{w}{L} \right] (V_{GS} - V_T)^2$$



$$I_D = \frac{1}{2} \mu_n C_{ox} \left[\frac{W}{L} \right] (V_{GS} - V_T)^2$$

$$= \frac{1}{2} \mu_n C_{ox} \left[\frac{W}{L + \Delta L} \right] (V_{GS} - V_T)^2$$

$$= \frac{1}{2} \mu_n C_{ox} \left[\frac{W}{L} \right] (V_{GS} - V_T)^2 \cdot \frac{1}{1 - \frac{\Delta L}{L}}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 \left(1 + \frac{\Delta L}{L} \right)$$

Let, since $\Delta L \propto V_{DS}$

$$\Rightarrow \Delta L = \lambda' V_{DS}$$

$$\frac{\Delta L}{L} = \frac{\lambda'}{L} V_{DS} = \lambda V_{DS}$$


Now,

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$$I_D' = I_D (1 + \lambda V_{DS}) \leftarrow \text{with channel length modulation}$$

Now
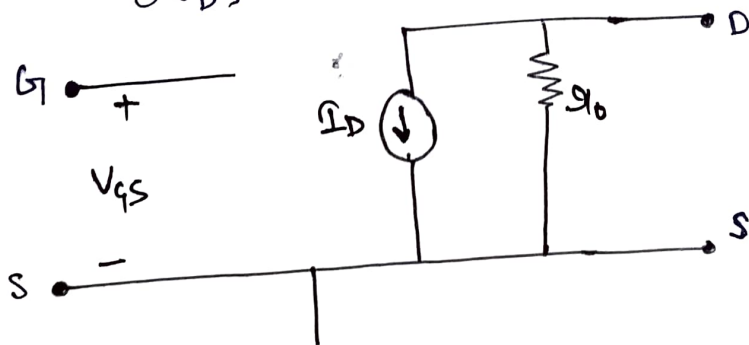
$$\frac{1}{g_o} = \frac{\partial I_D'}{\partial V_{DS}} = \lambda I_D \Rightarrow \boxed{g_o = \frac{1}{\lambda I_D}}$$



4. i) $V_{GS} < V_t \rightarrow \text{resistance} = \infty$

3.

$$I_D = K_n \left(\frac{W}{L} \right) \left(V_{OV} - \frac{1}{2} V_{DS} \right) V_{DS}$$

b $V_{GS} < V_t \rightarrow \text{resistance} = \infty$

5.

$$I_D = k_n \left(\frac{W}{L} \right) \left(V_{OV} - \frac{1}{2} V_{DS} \right) V_{DS}$$

$$V_{GS} > 0, V_{DS} = 0$$

effective voltage or overdrive voltage :- $V_{ov} = V_{GS} - V_t$

Magnitude of change in the channel $|Q| = C_{ox}(WL) \cdot V_{ov}$
 $\uparrow$
 oxide capacitance

$$\Leftarrow C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \leftarrow \text{oxide thickness}$$

$w \rightarrow$ channel width
 $L \rightarrow$ channel length

$$\epsilon_{ox} = 3.9 \epsilon_0 = 3.45 \times 10^{-11} \text{ f/m (for silicon oxide)}$$

$$C = C_{ox} WL$$

Now applying small V_{DS} also! —

Source $\rightarrow$ grounded

$$V_D \neq 0, \quad V_G \neq 0$$

flow of current $\rightarrow$ drain to source (i.d)

$$I_D = \frac{101}{\text{unit channel length}} = C_{ox} W V_{ov}$$

electric field establishes by V_{DS} across the channel length:-

$$|E| = \frac{V_{DS}}{L}$$

electron drift velocity $= \mu_n |E| = \mu_n \frac{V_{DS}}{L}$

$$i_D = \left[(\mu_n C_{ox}) \left(\frac{W}{L} \right) V_{ov} \right] V_{DS}$$

for small V_{DS} , channel behave like linear resistor
 which can be control by overdrive voltage
 in term of V_{GS} , do.

$$I_D = \left[(\mu_n C_{ox}) \left(\frac{W}{L} \right) (V_{GS} - V_t) \right] V_{DS}$$

conductance of channel

$$g_{DS} = (\mu_n C_{ox}) \left(\frac{W}{L} \right) V_{ov}$$

$$\text{or } (\mu_n C_{ox}) \left(\frac{W}{L} \right) (V_{GS} - V_t)$$

Process conductance $K_n' = \mu_n C_{ox}$ unit (A/V^2)

aspect ratio ($\frac{W}{L}$)


Transconductance $K_n = K_n' \left(\frac{W}{L} \right) = \mu_n C_{ox} \left(\frac{W}{L} \right) \rightarrow \text{unit } (A/V^2)$

$$g_{DS} = \frac{1}{g_{DS}} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right) V_{ov}}$$

$$= \frac{1}{(\mu_n C_{ox}) \left(\frac{W}{L} \right) (V_{GS} - V_t)}$$

signal } channel conductance
 = drain to source conductance
 (linear region).
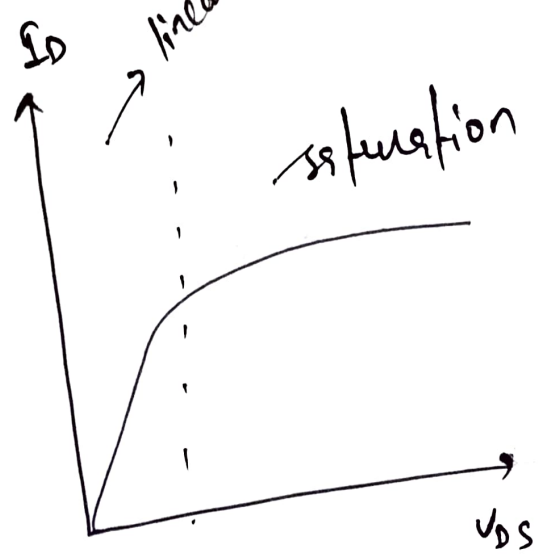
$$g_{ds} = \frac{\partial I_D}{\partial V_{DS}}, \quad \underset{\substack{\uparrow \\ \text{channel resistance}}}{g_{ds}} = \frac{1}{g_{ds}}$$




$$I_D = 2K \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]; \quad \leftarrow \text{in linear region, } V_{DS} < V_{GS} - V_T$$

for small V_{DS} , $\frac{V_{DS}^2}{2}$ ignored,

$$I_D = 2K \left[(V_{GS} - V_T) V_{DS} \right]$$
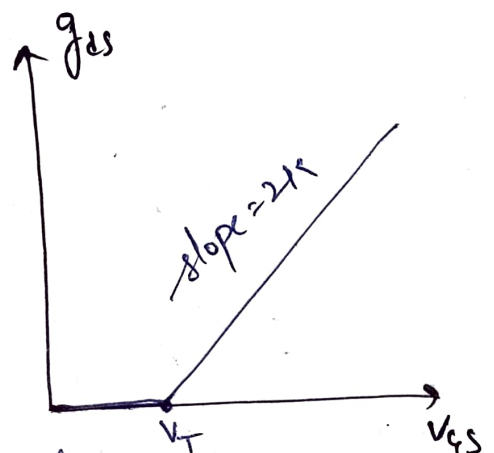
$$g_{ds} = \frac{\partial I_D}{\partial V_{DS}} = 2K(V_{GS} - V_T)$$



before V_T MOSFET in cutoff mode, there is no current channel conductance is zero.

Trans conductance :—

MOSFET acts as an amplifier in saturation mode

↳ small signal model


$$g_m = \frac{\partial I_D}{\partial V_{GS}}, \quad I_D = K(V_{GS} - V_T)^2 \rightarrow$$

$$g_m = 2K(V_{GS} - V_T), \quad K = \frac{\mu_n C_{ox} W}{2L}$$

all signal } channel conductance
 g_{ds} = drain to source conductance
 (linear region).

$$g_{ds} = \frac{\partial I_D}{\partial V_{DS}} \quad , \quad r_{ds} = \frac{1}{g_{ds}}$$

↑
channel resistance.

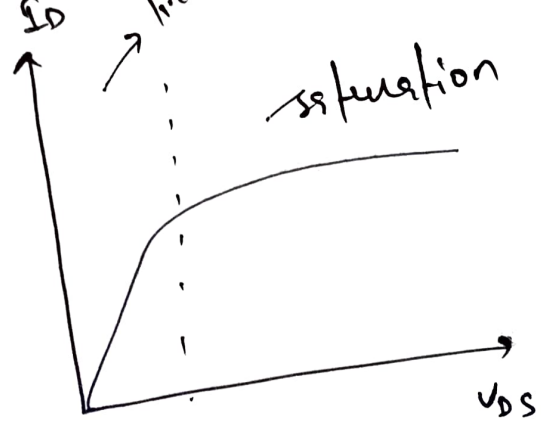


$$I_D = 2K \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]; \quad \text{in linear region, } V_{DS} < V_{GS} - V_T$$

for small V_{DS} , $\frac{V_{DS}^2}{2}$ ignored,

$$I_D = 2K \left[(V_{GS} - V_T) V_{DS} \right]$$
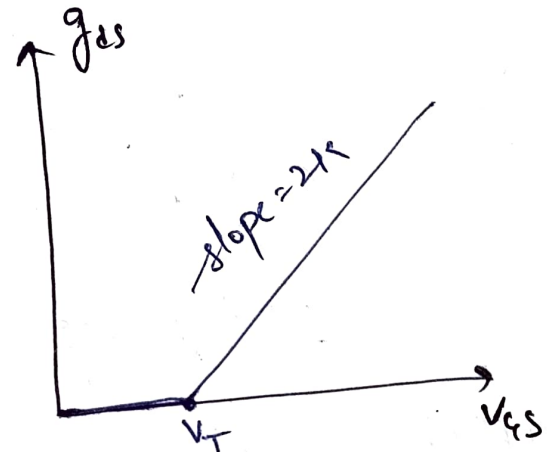
$$g_{ds} = \frac{\partial I_D}{\partial V_{DS}} = 2K(V_{GS} - V_T)$$



before V_T MOSFET in cutoff mode, there is no current, channel conductance is zero.

Trans conductance :-

MOSFET acts as an amplifier in saturation mode
 ↳ small signal mode

$$g_m = \frac{\partial I_D}{\partial V_{GS}} \quad , \quad I_D = K(V_{GS} - V_T)^2 \rightarrow$$

$$g_m = 2K(V_{GS} - V_T) \quad , \quad K = \mu_n C_{ox} \frac{W}{2L}$$

$$g_m = 2K \sqrt{\frac{I_D}{K}} = 2\sqrt{K I_D}$$

from ' I_D ' eq"

o/p resistance:- $r_d = \frac{\partial V_{DS}}{\partial I_D} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \text{high.}$

$$I_D = K(V_{GS} - V_T)^2 \underbrace{\left(1 + \lambda V_{DS}\right)}_{\text{from channel length modulation}}$$

$$\frac{\partial I_D}{\partial V_{DS}} = K \lambda (V_{GS} - V_T)^2 \approx \lambda I_D$$


$$r_d = \frac{1}{\lambda I_D}$$

Small Signal Model

Hybrid - pi - Model:-


↳ gate terminal:- oxide layer is present

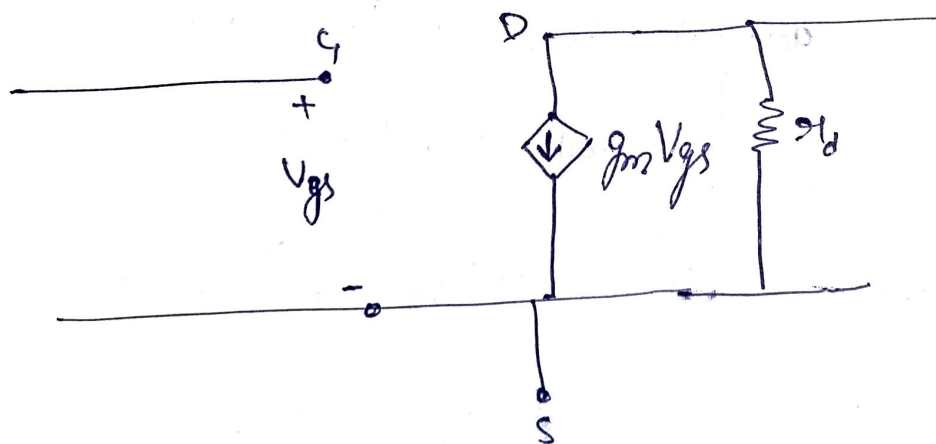↳ I_g or $I_{in} = 0$; $Z_{in} \rightarrow \infty$ (open ckt)




Model:-

Small signal alternate model

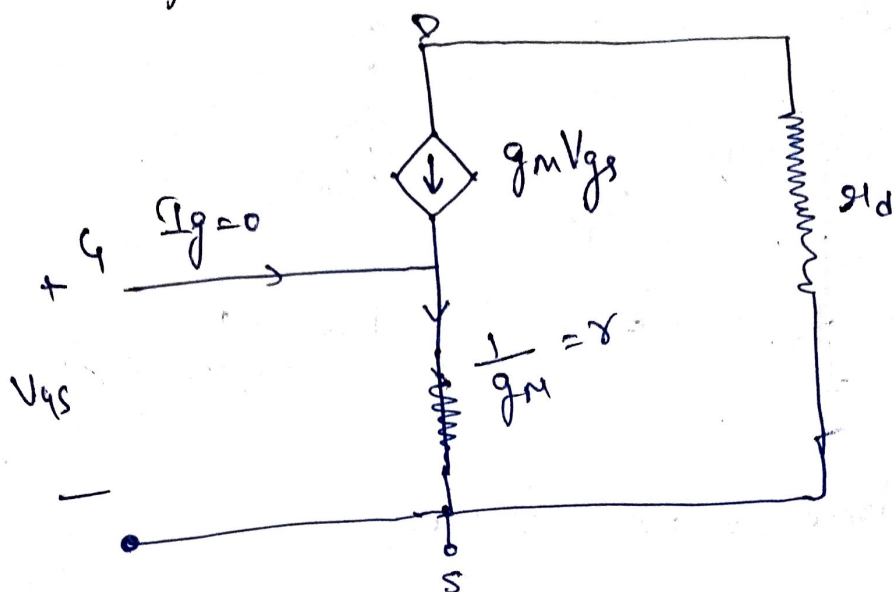


Common Source amplifier:- (highest voltage gain)

for dc analysis
short ac, open ckt
Cap.

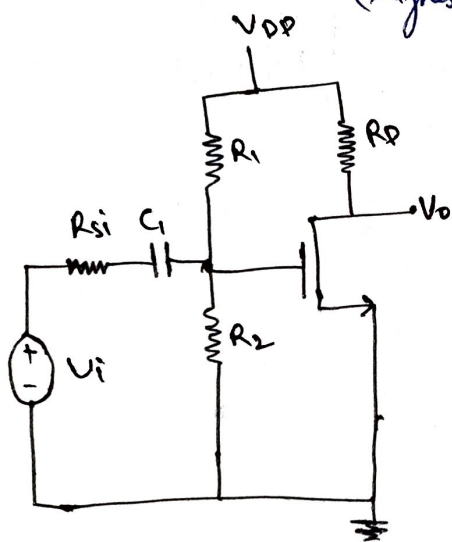

≡

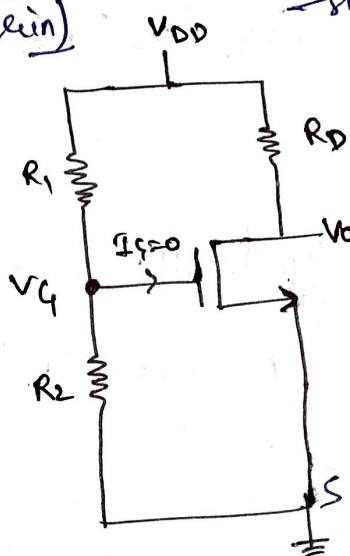

$$V_G = \frac{V_{DD} R_2}{R_1 + R_2}$$

$$V_{GS} = V_G - V_S = V_G$$

↑ grounded.


$$I_D = K(V_{GS} - V_T)^2$$

(saturation)

$$g_m = 2\sqrt{K I_D}$$

for ac analysis:-

ground V_{DD} , short all cap.

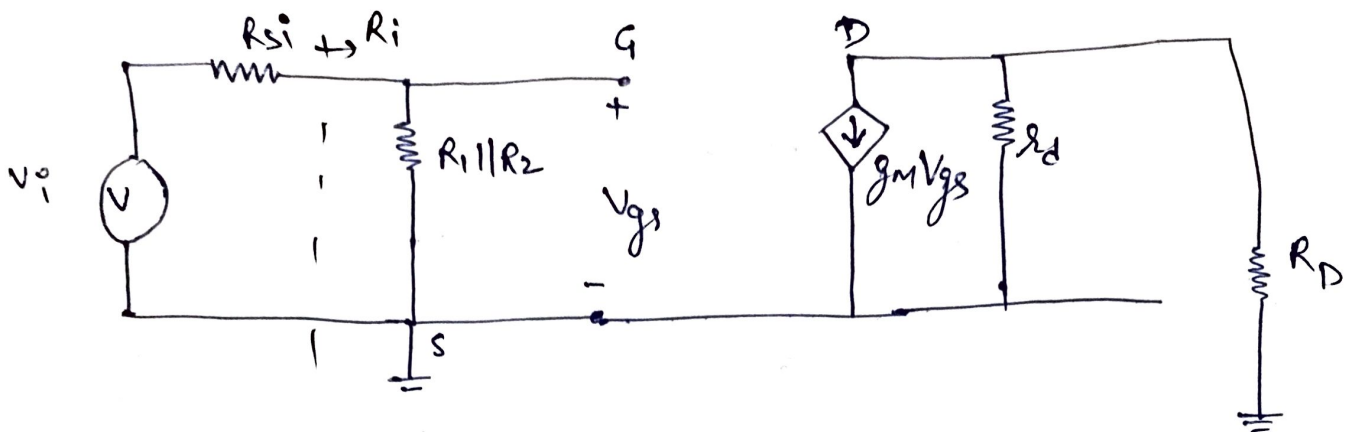

Input resistance = $R_i = R_1 \parallel R_2$

output resistance :- $R_{out} = r_o \parallel R_D \approx R_D$

$$V_o = -g_m V_{gs} (r_o \parallel R_D); \quad V_{gs} = V_i \left(\frac{R_1 \parallel R_2}{R_{si} + R_1 \parallel R_2} \right)$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m (r_o \parallel R_D) (R_1 \parallel R_2)}{R_{si} + (R_1 \parallel R_2)}$$

if $R_{si} = 0$

$$A_v = -g_m (r_o \parallel R_D)$$

Common Source Amplifier


57

passing $R_s \rightarrow$ gain $\downarrow$
(-ve feedback)


step 1: dc analysis:- oc C_p

$$I_D = ? , g_m = 2\sqrt{K I_D}$$

$$r_d = ?$$

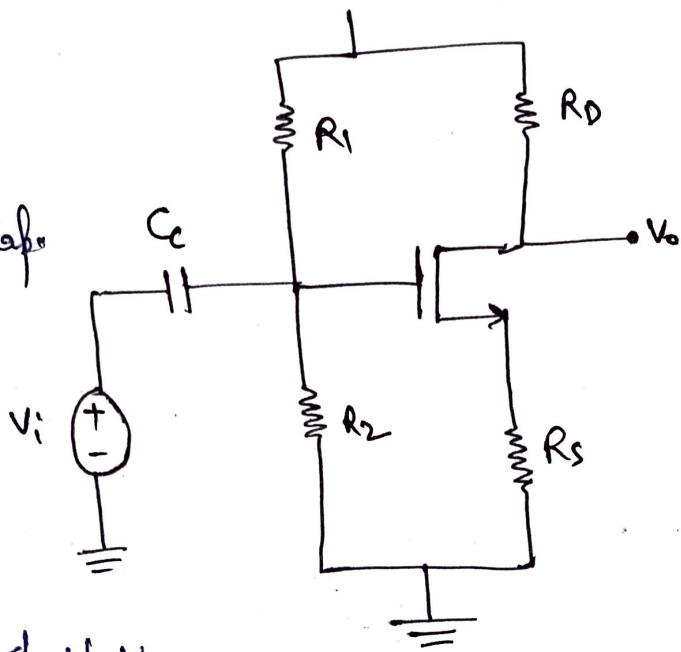

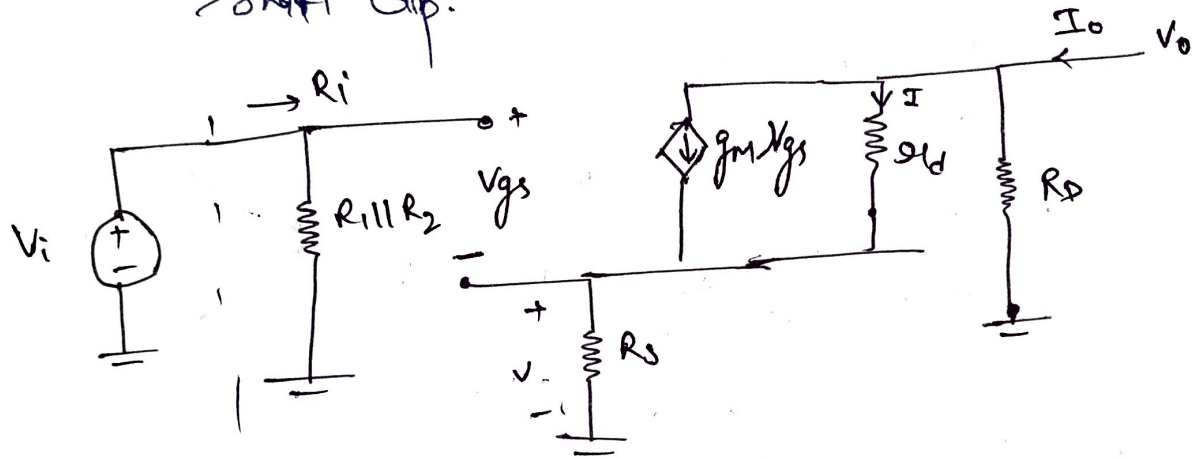step 2: - ac analysis short V_{DD}
short C_p .



$$v_{gs} + v = v_i$$

$$v_i = 0, v = -v_{gs}$$

small signal model

input resistance, $R_i = R_1 || R_2$

output resistance, $R_o = \frac{v_o}{I_o} \Big|_{v_i = 0}$

$$I_o = \frac{v_o}{R_D} + \frac{v_o - v}{r_d} + g_m v_{gs}$$

$$= \frac{v_o}{R_D} + \frac{v_o - v}{r_d} - g_m v$$

$$v = (g_m v_{gs} + I) R_s$$

$$= -g_m v R_s + \frac{v_o - v}{r_d} R_s$$

$$v \left[1 + g_m R_s + \frac{R_s}{r_d} \right] = \frac{v_o R_s}{r_d}$$

$$V = \frac{V_o R_s}{r_d}$$

$$1 + g_m R_s + \frac{R_s}{r_d}$$

$$\Rightarrow I_o = \frac{V_o}{R_D} + \frac{V_o}{r_d} - V(g_m + \frac{1}{r_d})$$

$$V_o \left[\frac{1}{R_D} + \frac{1}{r_d} - \frac{(g_m + \frac{1}{r_d}) \left(\frac{R_s}{r_d} \right)}{1 + g_m R_s + \frac{R_s}{r_d}} \right]$$

Ignore r_d , $\frac{1}{r_d} \rightarrow 0$

$$R_{out} \approx R_D$$

Voltage gain (A_v), Ignore r_d

$$V = g_m V_{gs} R_s; \quad V_i = V_{gs} + V \Rightarrow V_{gs} = (1 + g_m R_s)$$



$$V_o = -g_m V_{gs} R_D; \quad A_v = \frac{V_o}{V_i} = \frac{-g_m R_D}{1 + g_m R_s}$$

Common Drain or source follower:-

1:- for dc analysis, $I_D = ?$

$$g_m = 2\sqrt{I_D}$$

2:- ground V_{DD} ,
short cap.

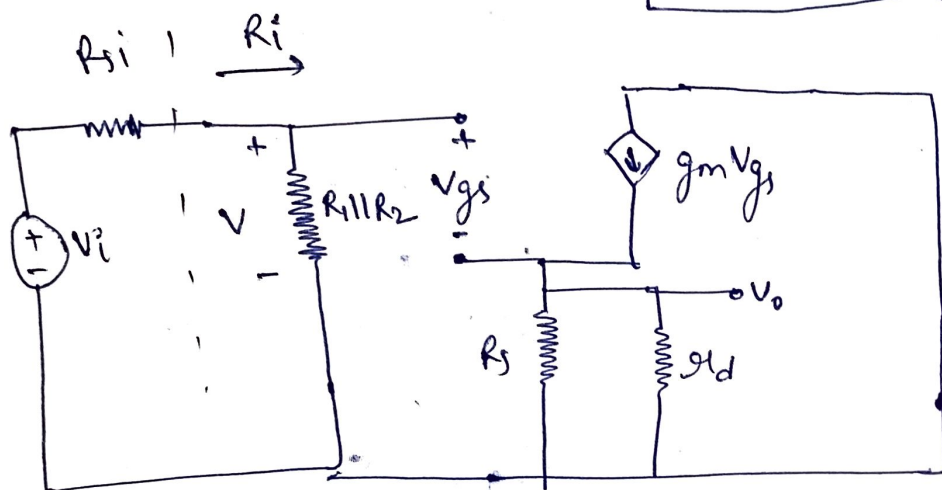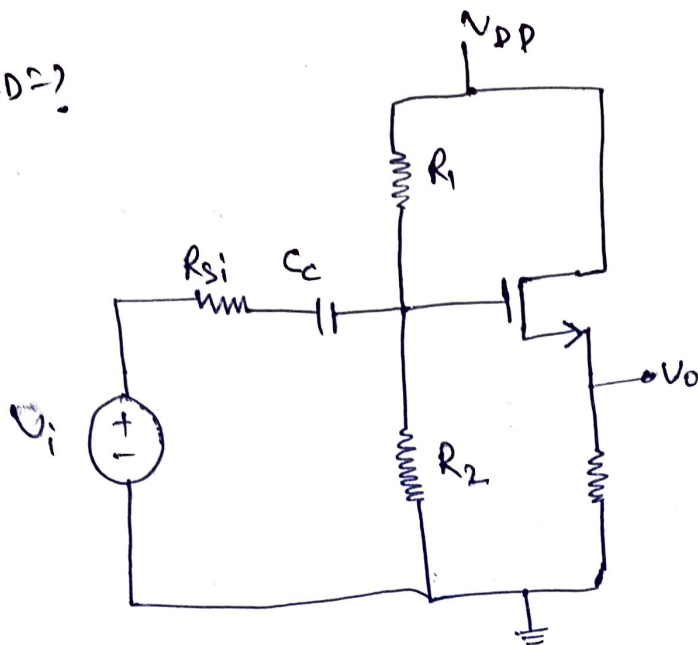

Input resistance $R_i = R_1 \parallel R_2$

Small signal model:-

$$\text{voltage gain} = \frac{V_o}{V_s}$$

$$V_o = g_m V_{gs} (R_d \parallel R_s)$$

$$V = V_s \times \left(\frac{R_1 \parallel R_2}{R_{si} + (R_1 \parallel R_2)} \right) = V_{gs} + V_o = V_{gs} (1 + g_m (R_d \parallel R_s))$$

$$V_s = V_{gs} (1 + g_m (R_d \parallel R_s)) \times \frac{R_{si} + (R_1 \parallel R_2)}{(R_1 \parallel R_2)}$$

$$A_{vs} = \frac{V_o}{V_s} = \underbrace{\frac{g_m (R_d \parallel R_s)}{1 + g_m (R_d \parallel R_s)}}_{A_v} \left[\frac{R_1 \parallel R_2}{R_{si} + R_1 \parallel R_2} \right]$$

$$A_{vs} = A_v \quad \text{if } R_{si} = 0$$

$$\underline{A_v < 1}$$

output resistance: -

$$R_{out} = \frac{V_o}{I_o} \Big|_{v_{in}=0}$$

$$I_o - g_m V_o = \frac{V_o}{R_s} + \frac{V_o}{R_d}$$

$$I_o = \left(g_m + \frac{1}{R_s} + \frac{1}{R_d} \right) V_o$$

$$\frac{V_o}{I_o} = R_{out} = R_s \parallel R_d \parallel \frac{1}{g_m}$$

$$I_o + g_m V_{gs} = V_o \left(\frac{1}{R_s} + \frac{1}{R_d} \right)$$

$$V_o = 0 = V_{gs} + V_o$$

$$\boxed{V_{gs} = -V_o}$$